

Analog-to-digital conversion (ADC)

MEC100x-Lectures 7_1

Energy, Power and Intelligent Control

School of Electronics, Electrical Engineering and Computer Science

Ashby Building

Queen's University Belfast


Aims of this lecture are:

1. Why ADC?
2. Sample/Hold
3. ADC Essentials
4. Converter errors, converter resolution, conversion time, Quantization Interval
5. Analog input signal ranges and resolution
6. Parallel or Flash ADC

Good understanding Analog Vs Digital

- ❑ Many of our electronic devices are digital circuits; robotic systems- industrial plants- Daily Life systems
- ❑ These kind of electronic devices use analog sensors to interact with the real world/ industrial processes.
- ❑ Analog signal provides a signal that can be between 0 volts and give a maximum voltage like 5 volts or 9 volts.

Detecting

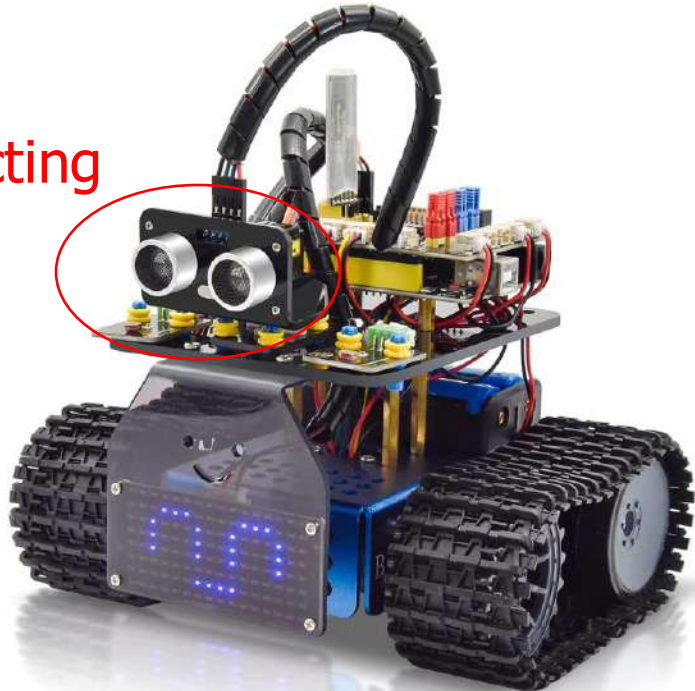


LDR resistance- Light Sensor





Analog Sensors

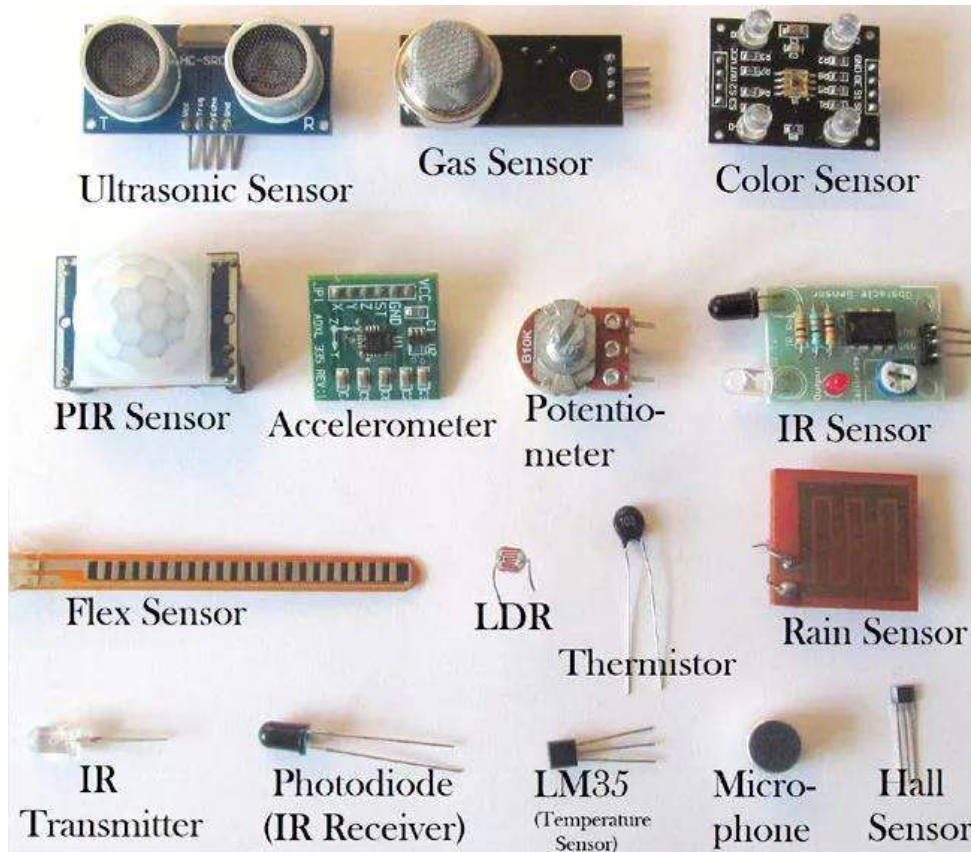- ❑ Sensors produce continuous analog signal. **Analog signals: There are continuity in the signal.**
- ❑ Standard ranges of analog signal are: 5V DC, 10V DC, 0 to 20 mA, 4 to 20 mA,...
- ❑ There are various types of analog sensors such as **temperature, humidity, colour, pressure, light, sound sensor, ultrasonic sensor and gas sensor, etc.**



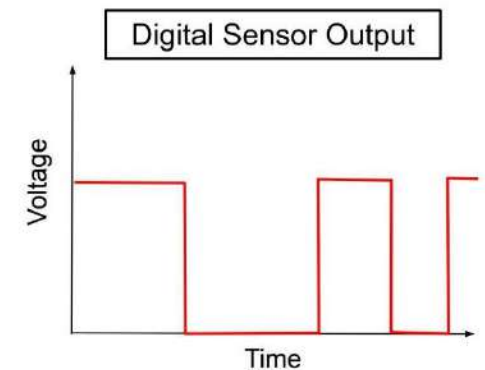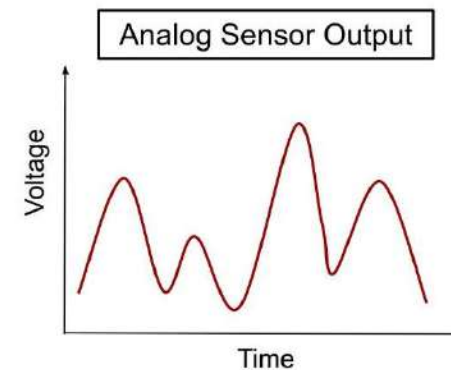Zero is representing: 0V
1 is representing: 5/ 10 Volts



<https://www.smlease.com/entries/automation/what-are-different-types-of-sensors-and-their-applications/>

<https://pijaeducation.com/arduino/sensor/>

Binary

- ❑ Binary is a series of 1 and 0 **for example(4 bits: 1000, 0110, 0001, 1101,1111,...).**

We can compare:

- ❑ Digital **to a light switch** turning the light either **ON/OFF.**
- ❑ Analog would be like **a dimmer switch that is** able to set the light level to any brightness between **maximum and OFF.**

Watch this video clip:




video

Why ADC?

- Digital Signal Processing is more popular
- Low impact of noise on these signals
- Computer and Microcontroller processing are binary and digital

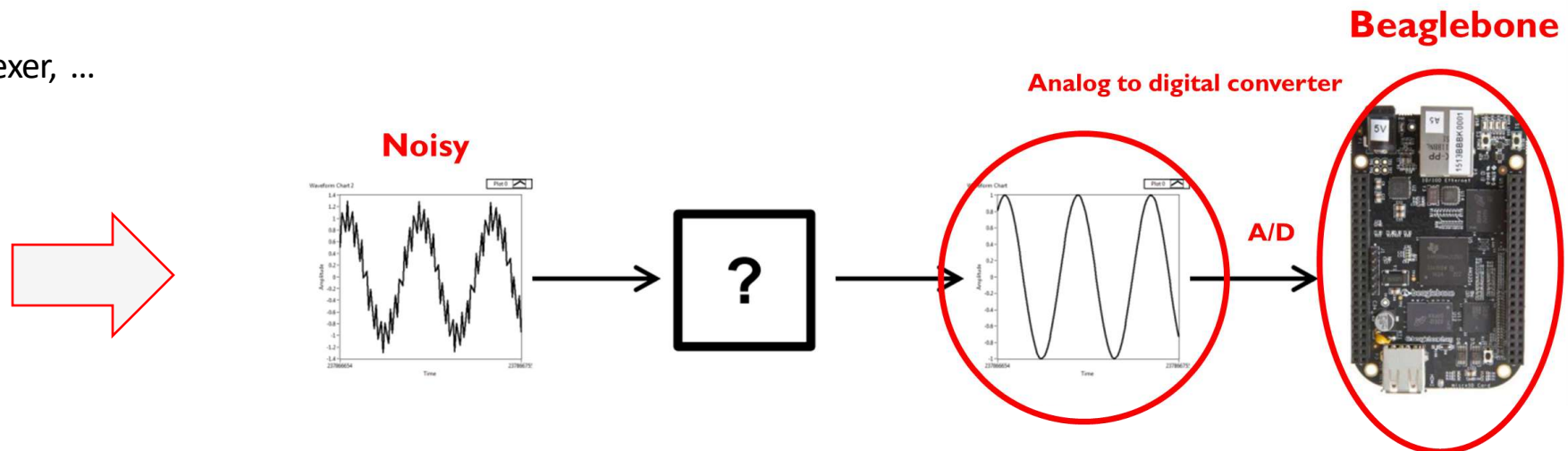- Data from real world are typically analog signal
- Needs conversion system from raw measurements to digital data
- Digital Signal Processing Consists of
 - Amplifier, Filters
 - Sample and Hold Circuit, Multiplexer, ...
 - ADC, DAC



ADC and DAC

Digital-to-Analog Conversion (DAC)

- D/A; Converts a binary value to a scaled 'analog' voltage
- D/A is used for controlling systems that require an analog actuators input such as :
 - DC servo motor
 - Resistive heater, etc.


Analog-to-Digital Conversion (ADC)

- A/D; Converts a continuous analog voltage into discrete binary values
- A/D is used to translate continuous physical phenomena into a language the computer understands **(Binary Code)**.

ADC

Analog signals


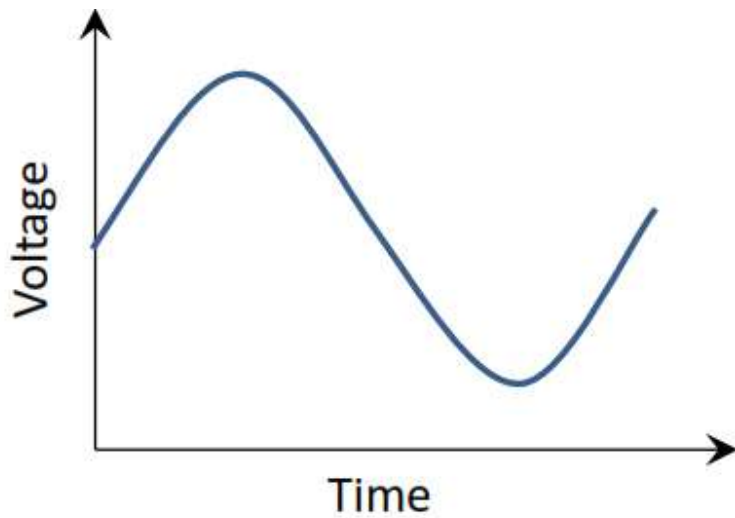
- Any **continuous signal- smooth continuous slope** that a time varying variable of the signal is a representation of some other **time varying quantity**.
- **Analog signal** is a form of electrical energy (voltage, current or electromagnetic power) that there is a linear relationship between electrical quantity and the value on each time.



0001
0010
0011
0101
....

Signals:

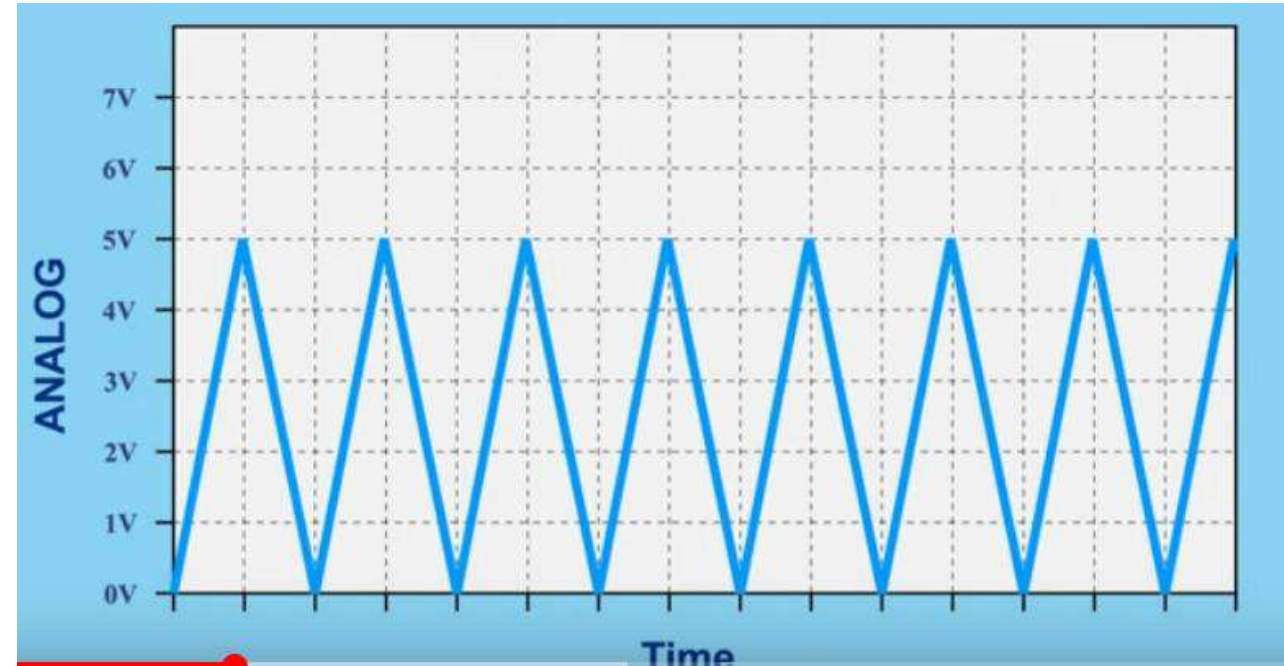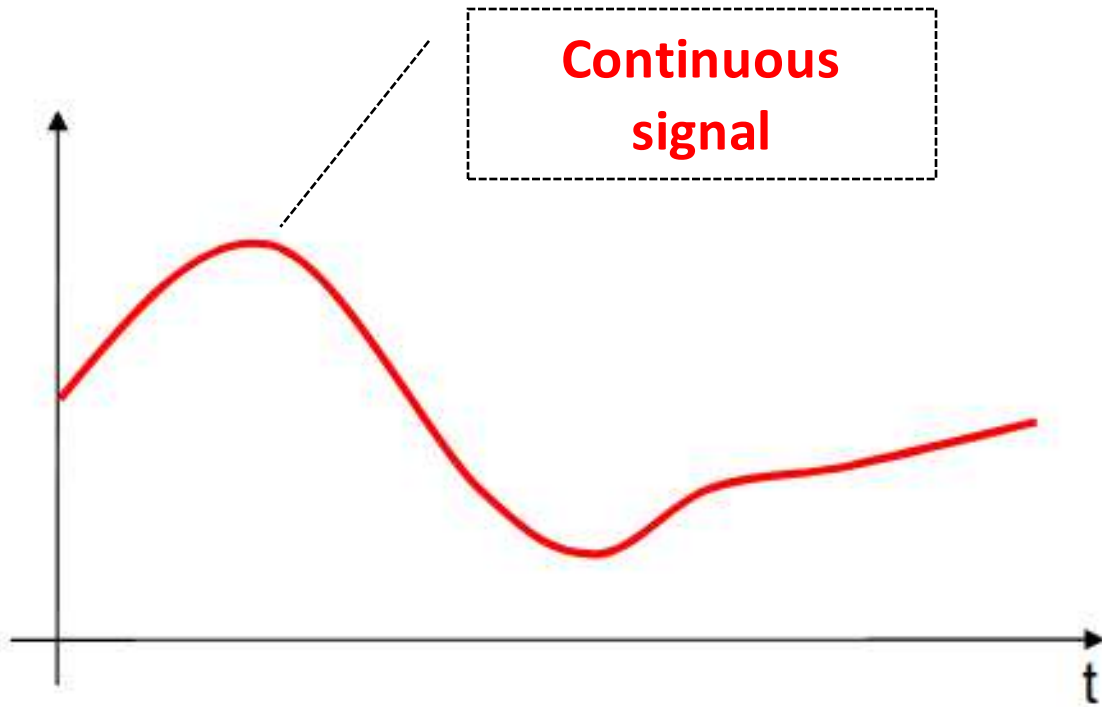continuous signal- smooth continuous slope





<https://www.youtube.com/watch?v=g4BvbAKNQ90>

<https://slideplayer.com/slide/4584344/>

The Waveform of a digital signal changes in steps with a finite number of steps equal to the ADCs resolution divided between 0 Volts and the maximum voltage. Signal change at each step goes low to high and high to low

3-bit ADC 2^n step

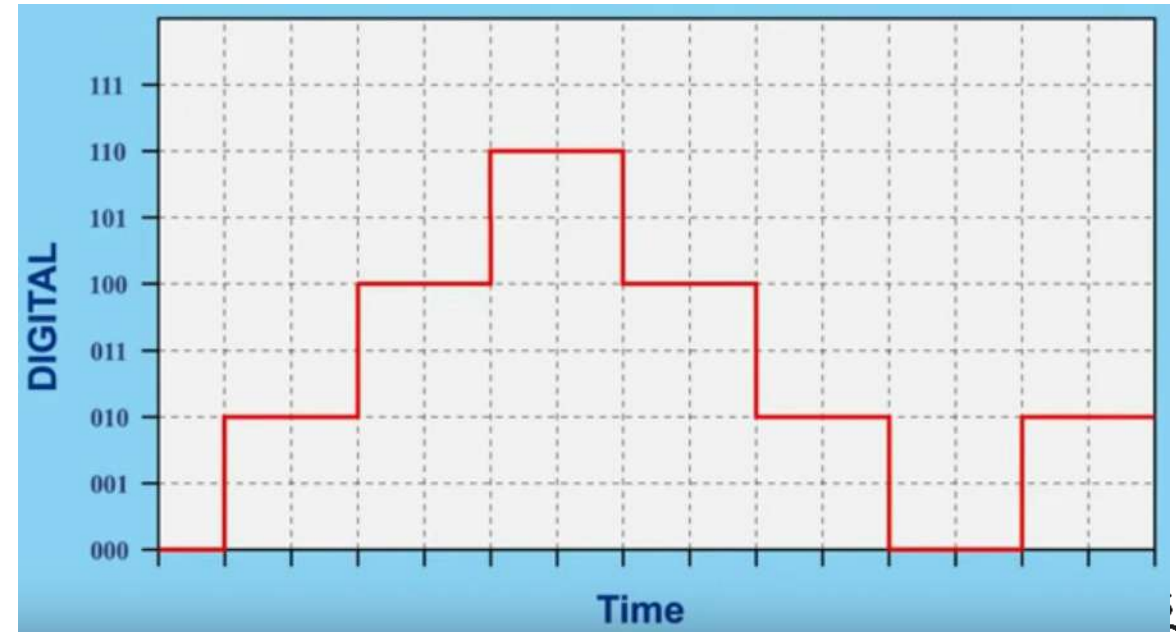
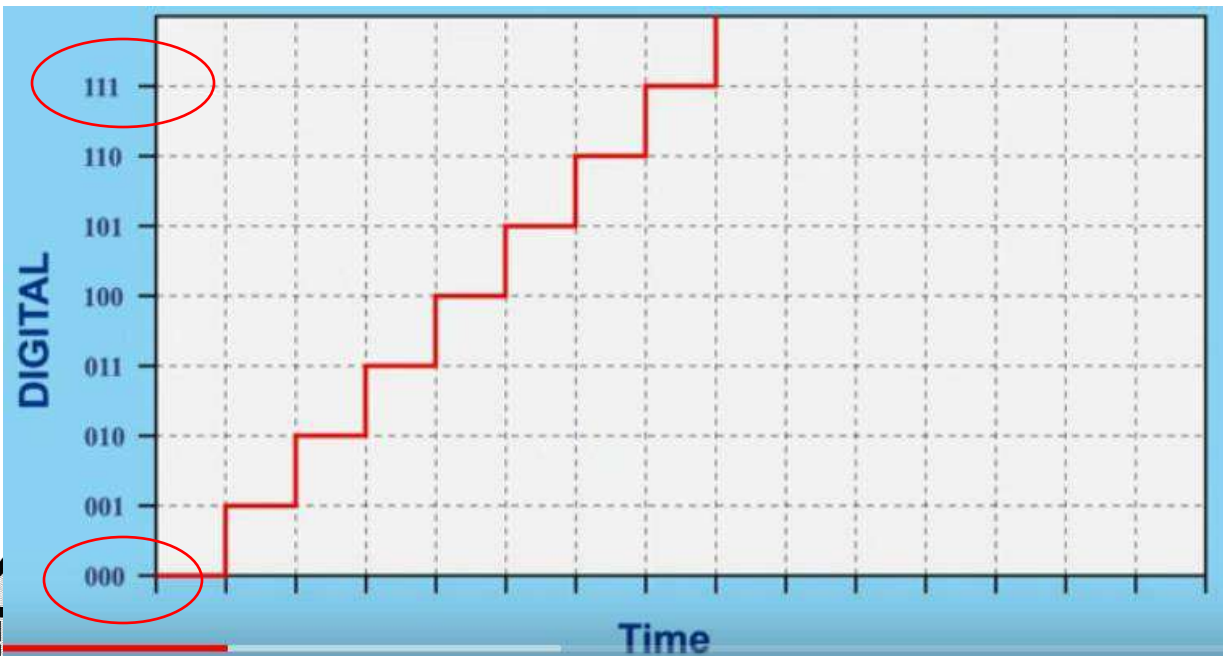


ADC



Digital signals

- Consist of only two states
- Binary states
- ON and OFF
- Computers can only perform processing on digitalized signals.

Binary states

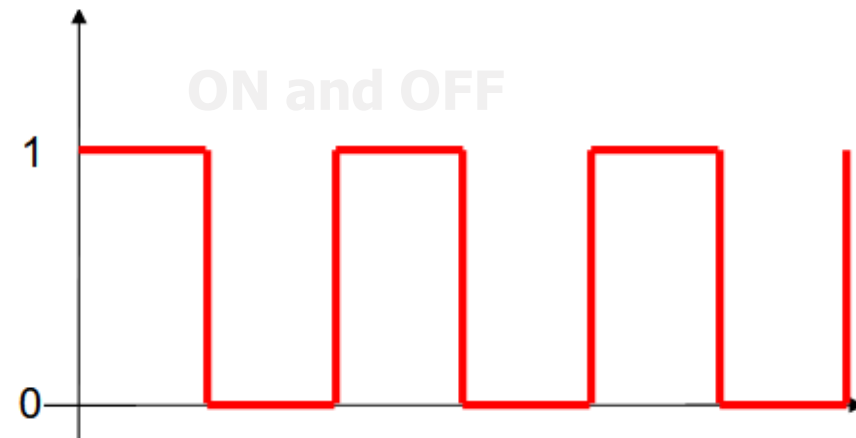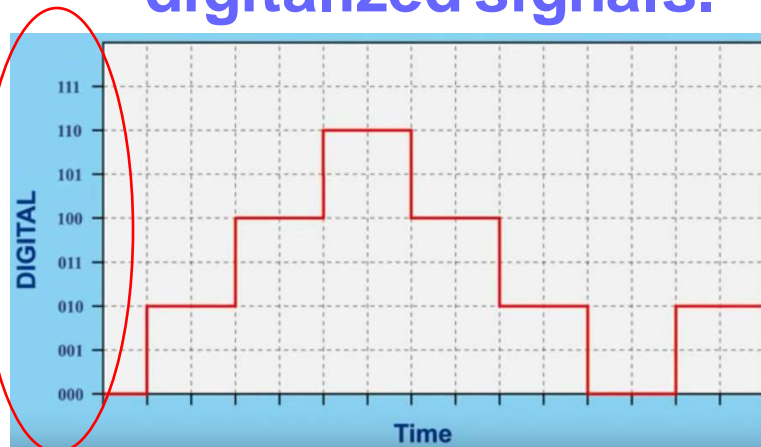

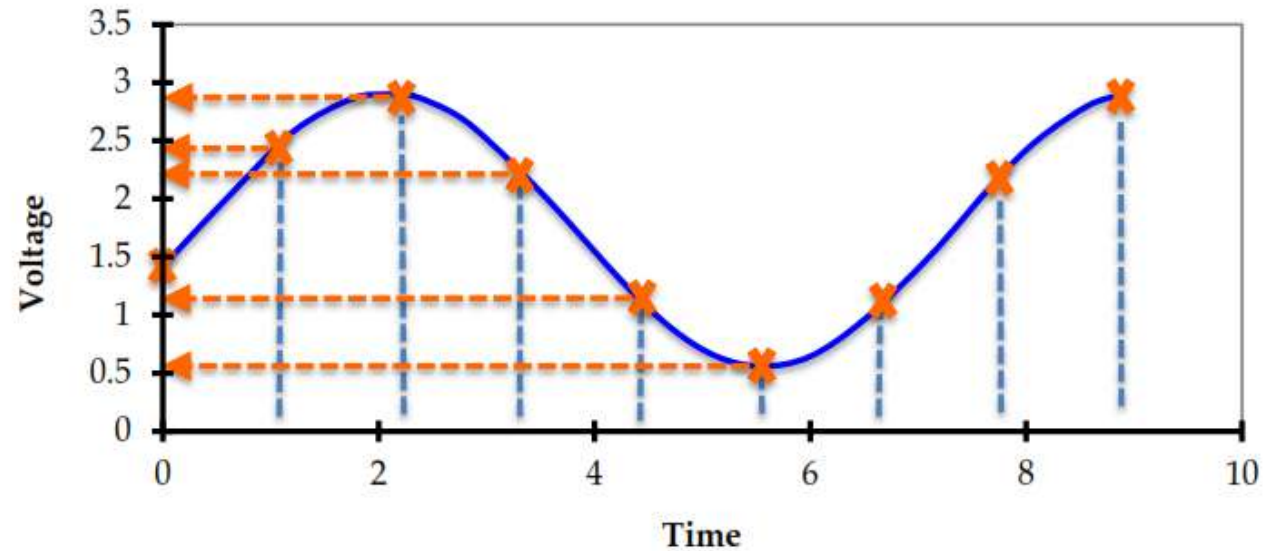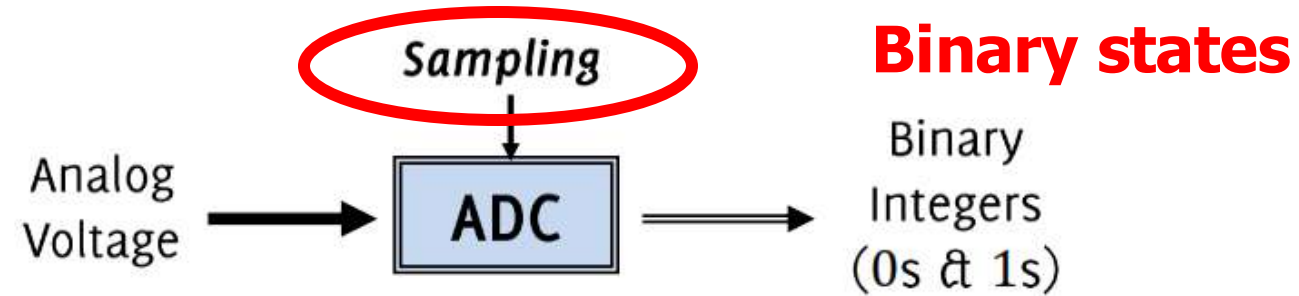A/D Conversion Converts analog input into digital values




<https://engineering.purdue.edu/ME588/LectureNotes/Unit5a--ADConversion.pdf>

Two main steps of process

1- sampling and holding


- **2- quantization and coding**

High frequency switch


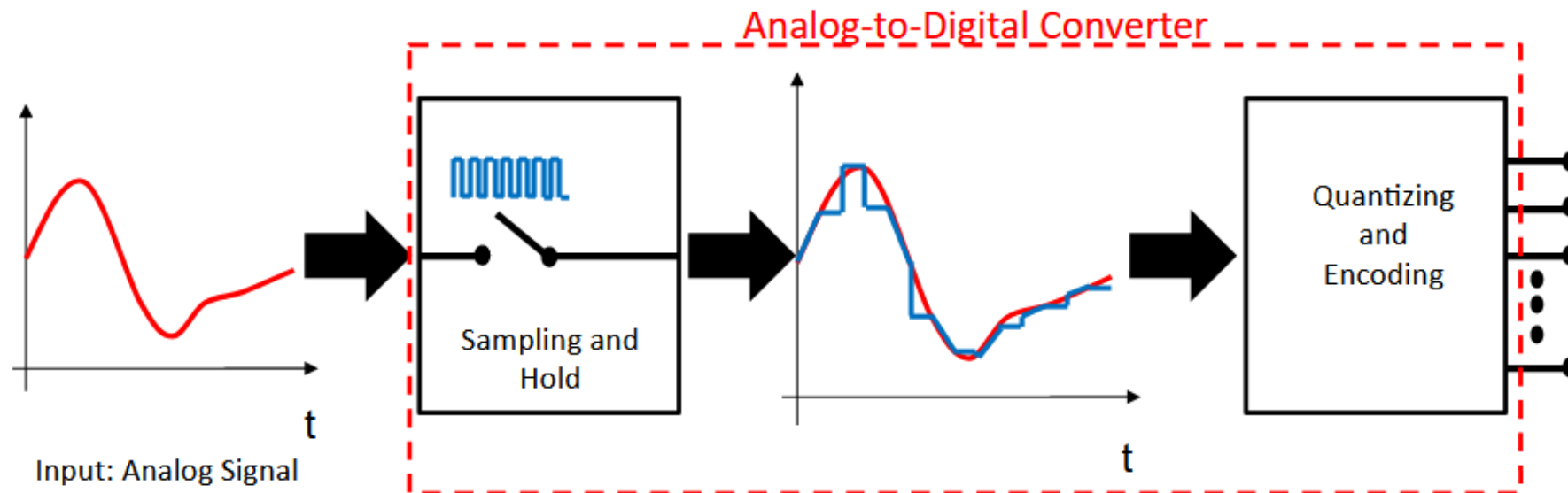


ADC Process

1- sampling

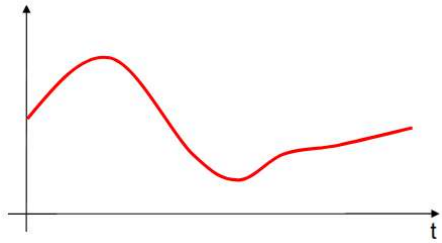

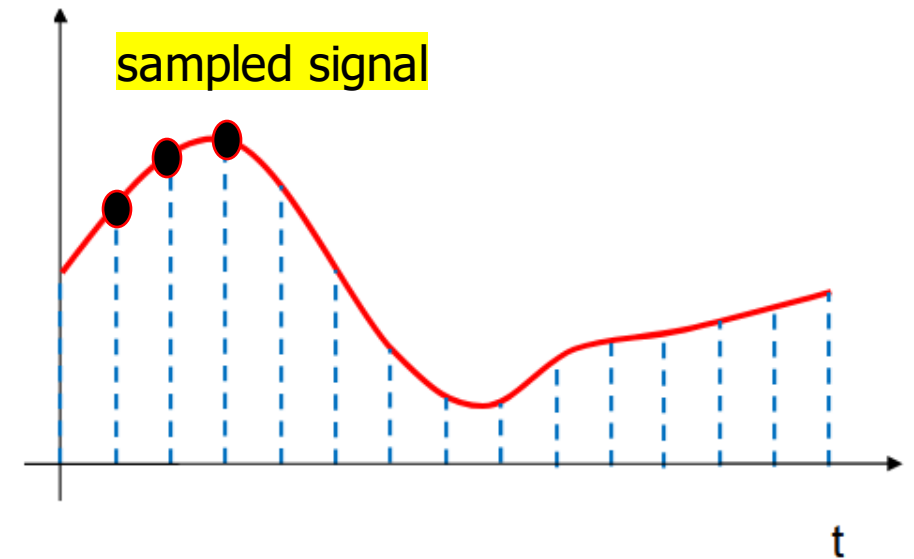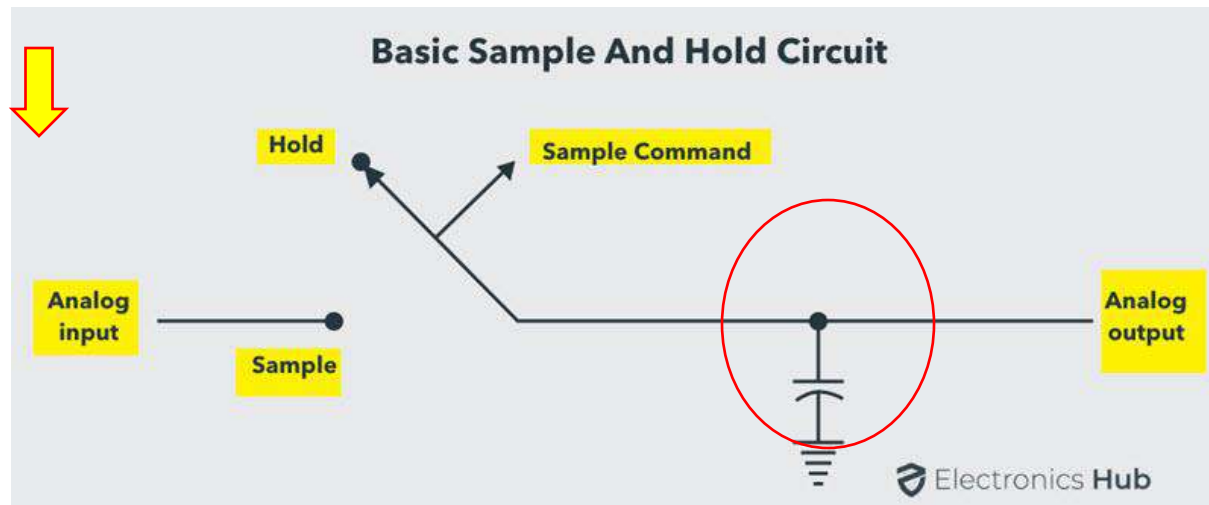- Measuring analog signals at **uniform time intervals (T_s)**
(Ideally twice as fast as what we are sampling)




ADC Process

1- sampling

- ❑ Digital system works with discrete states
- ❑ Taking a sample from each location.

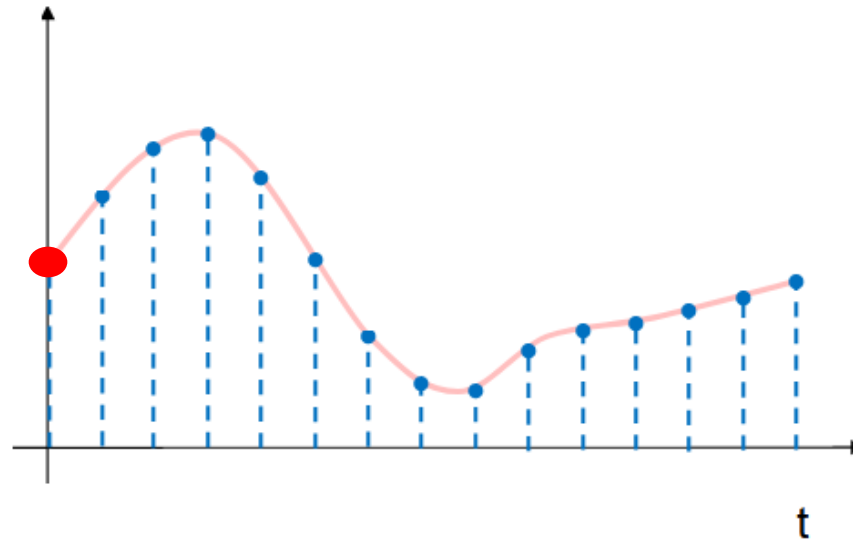T_s = Uniform time step
 T_s = Sampling time period





<https://slideplayer.com/slide/4584344/>

ADC Process

1- Holding

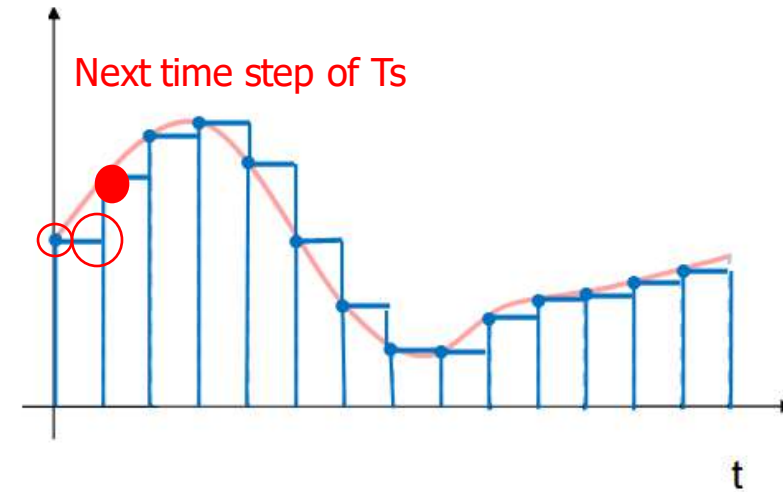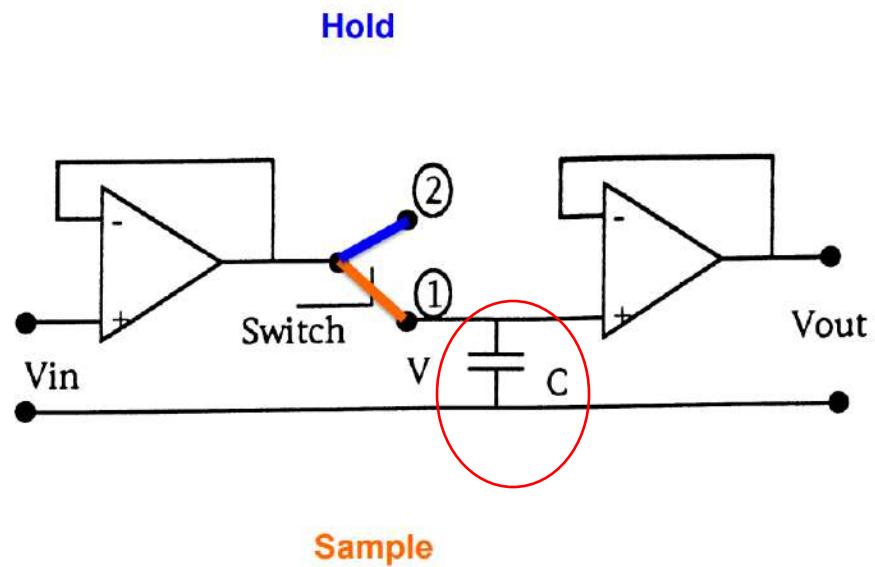- ❑ Reflects sampled and hold signal
- ❑ Digital approximation



<https://slideplayer.com/slide/4584344/>

<https://engineering.purdue.edu/ME588/LectureNotes/Unit5a--ADConversion.pdf>

Analog to Digital Conversion



Process of converting an analog signal to a digital number



Three step procedure



Sampling (sample and hold)



Quantization



Coding

ADC Essentials


Basic I/O Relationship

ADC is a Rationing System

x = Fraction: $0 \sim 1$
Analog input / Reference

n bits ADC

Number of discrete output level : 2^n

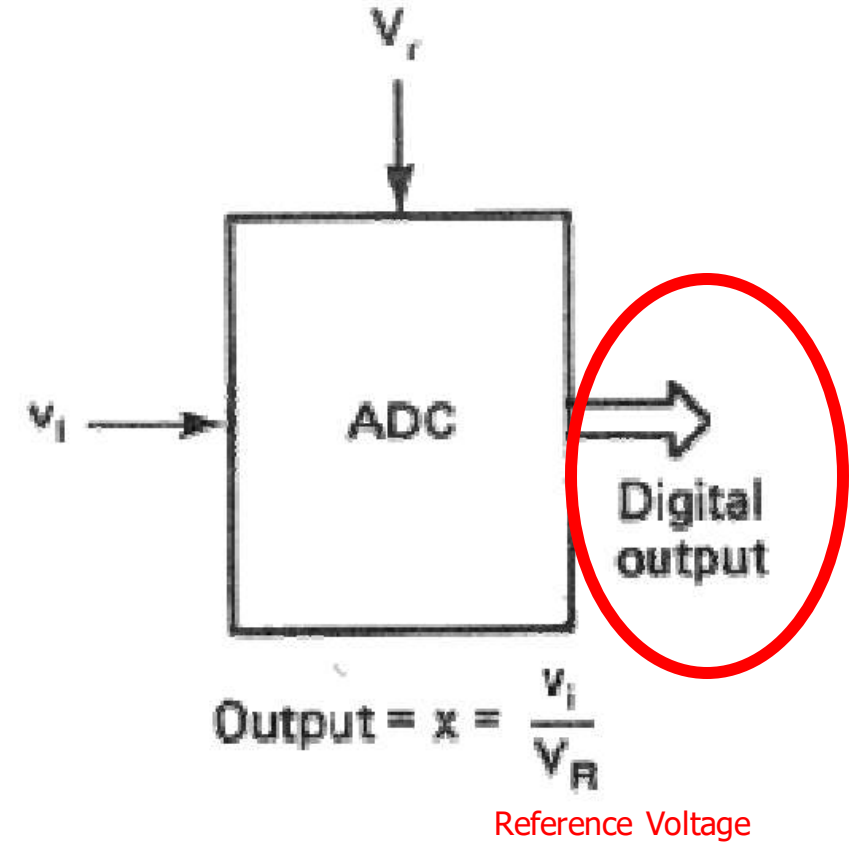

Quantization

➤ Separate the input signal into a discrete states with K increments

•
❑ $K = 2^n$ n is the number of bits

• Analog size Quantization


❑ $Q = \text{LSB} = (V_{\text{max}} - V_{\text{min}}) = \text{FS} / 2^n$

• Q is Resolution

Quantization Error


❑ $\pm 1/2 \text{ LSB}$

❑ Reduced by increasing n

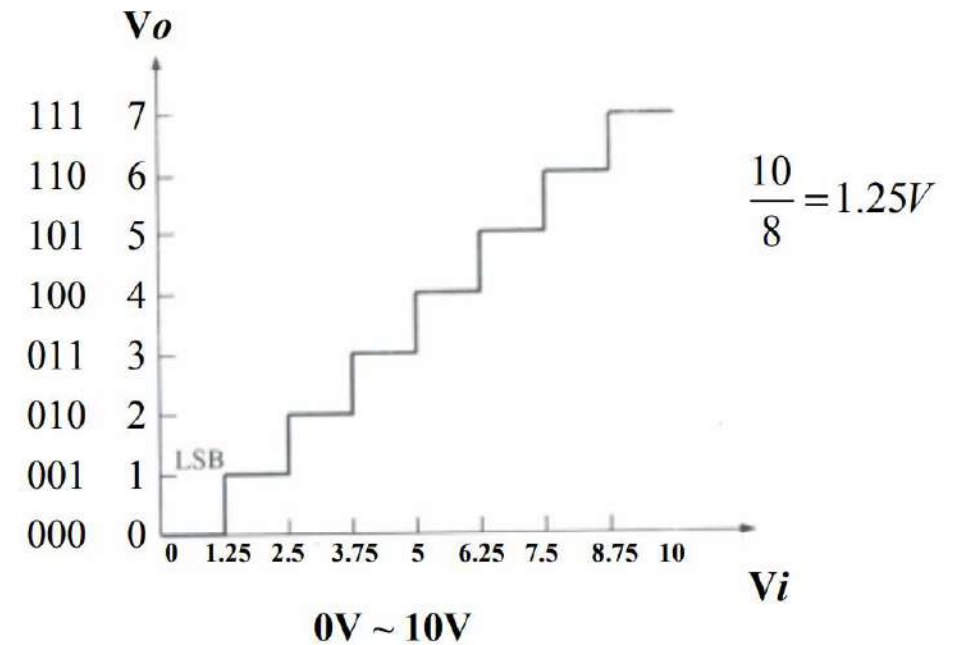


Quantization & Coding

Apply 2 bit coding

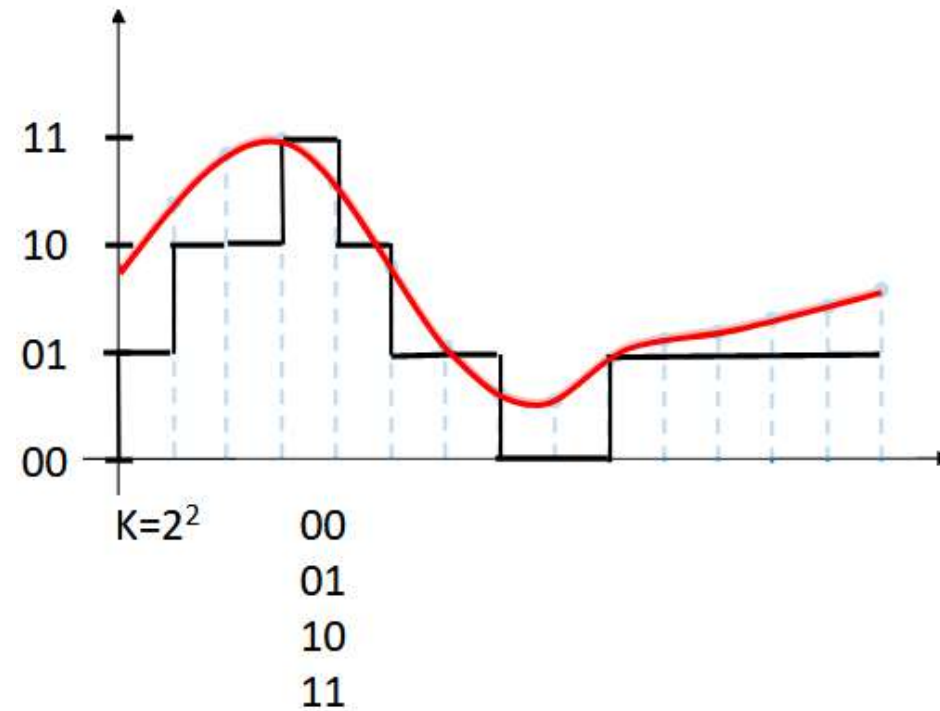


Quantization & Coding

Apply 3 bit coding

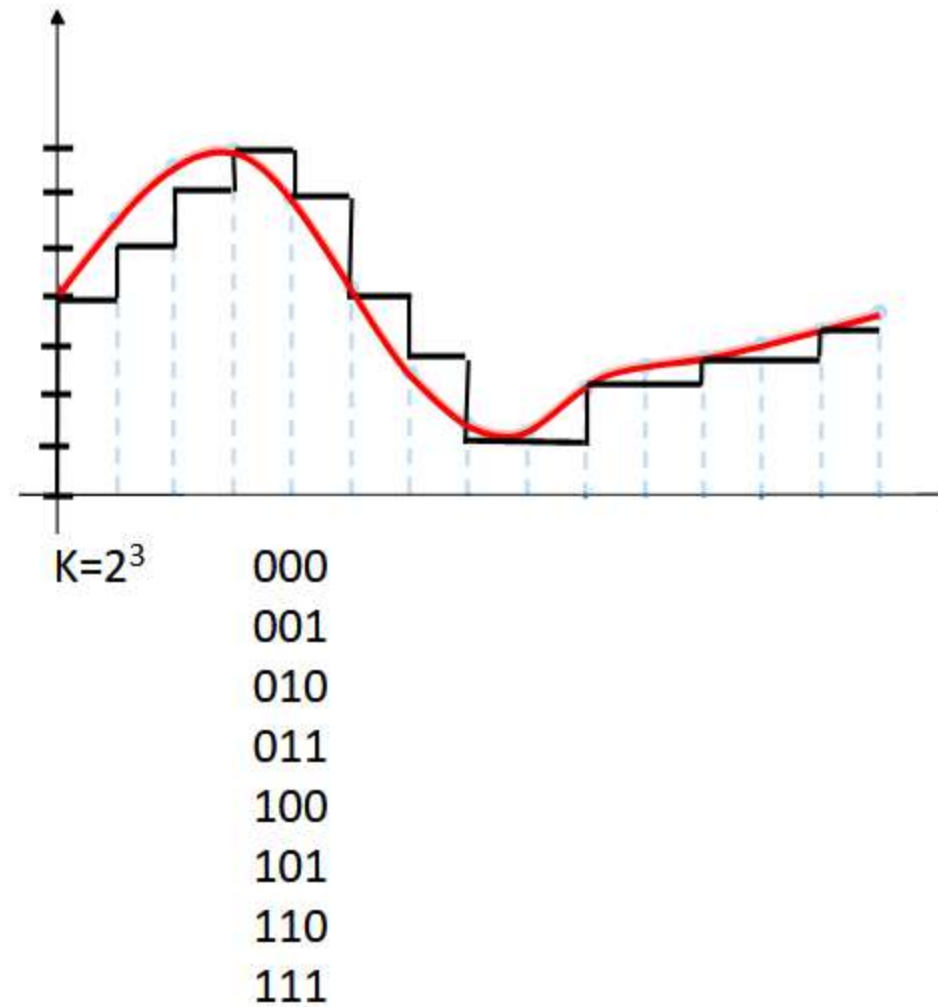


Converter Errors

Offset Error

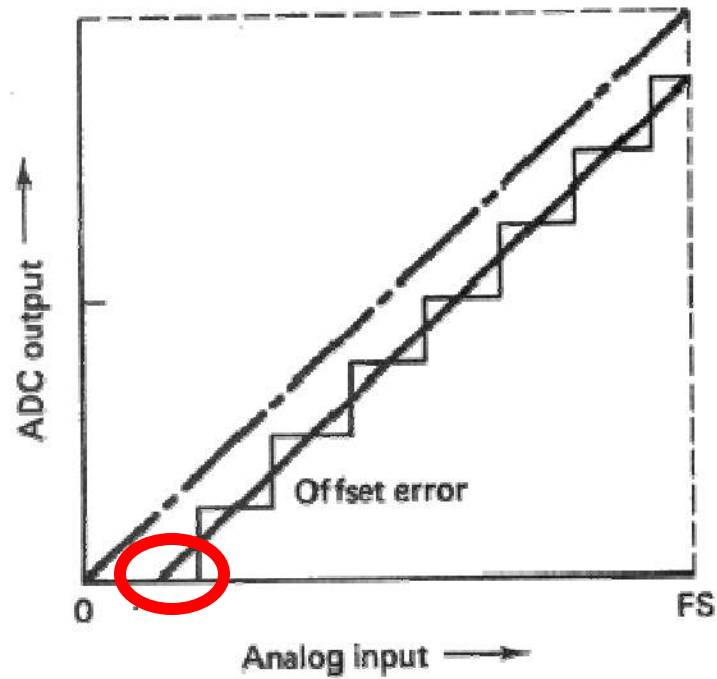


Can be eliminated by initial adjustments

Gain Error

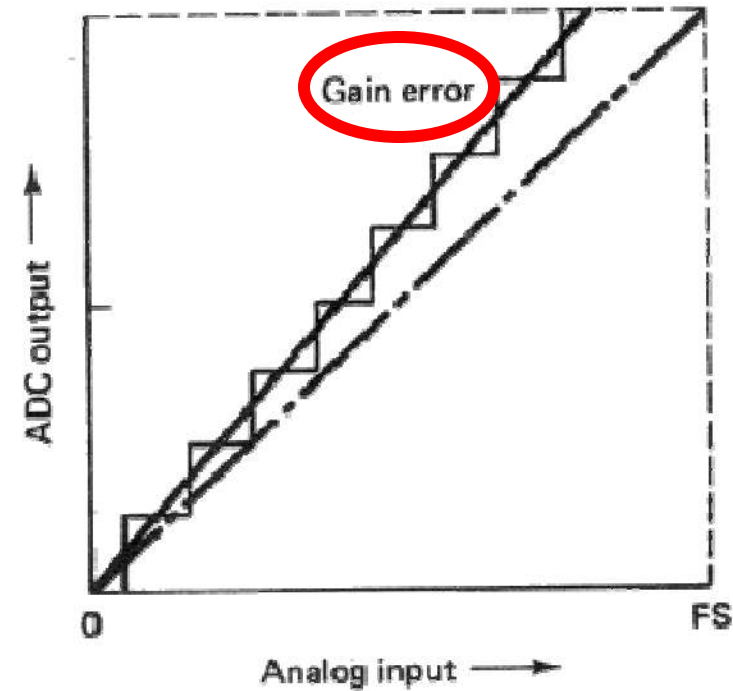


Converter Errors

Integral Linearity Error

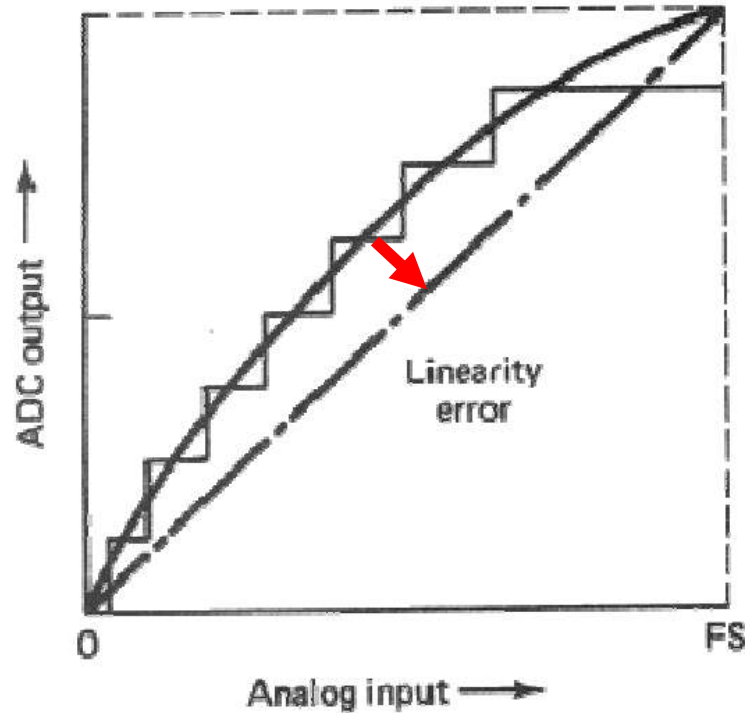

Differential Linearity Error

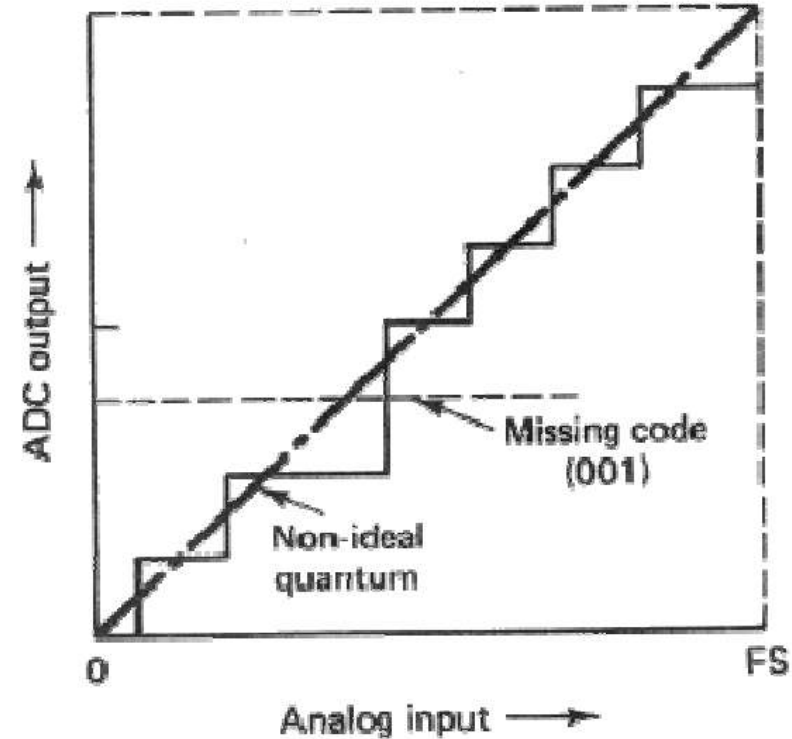

❑ Nonlinear Error: Hard to remove

ADC Essentials

❑ Converter Resolution

- ❑ The **smallest change required in the analog input** of an ADC **to change its output code** by one level

❑ Converter Accuracy

- ❑ The difference between **the actual input voltage** and the full-scale weighted equivalent of the binary output code.
- ❑ Maximum sum of all converter errors including quantization error.

❑ Conversion Time

- ❑ **Required time (t_c) before** the converter can provide valid output data

❑ Converter Throughput Rate

- ❑ The number of times the input signal can be sampled maintaining full accuracy
- ❑ Inverse of the total time required for one successful conversion
- ❑ Inverse of Conversion time if No S/H(Sample and Hold) circuit is used

Analog Input Signal

- Typically, Differential or Single-ended input signal of a single polarity

- Typical Input Range 0 ~ 10V and 0 ~ 5V

- Matching input signal and input range

- Pre-scaling input signal using OP Amp


- In a final stage of preconditioning circuit

- By proportionally scaling down the reference signal

- If reference signal is adjustable

Inputs/Outputs and Analog Reference Signal

I/O of typical ADC

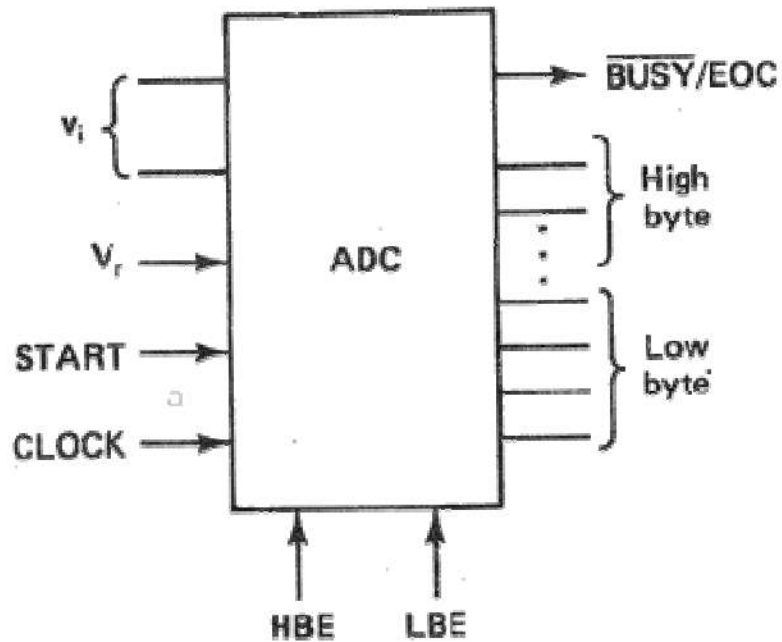

ADC output

- ❑ 8 and 12 bits are typical
- ❑ 10, 14, 16 bits also available

Errors in reference signal

- **From**
 - ❖ Initial Adjustment
 - ❖ Drift with time and temperature
- **Cause**
 - ❖ Gain error in transfer characteristics


Sampling rate:

- Sampling occurs when the input signal is changing much faster than the sample rate

Nyquist rule:

- Use a sampling frequency at least twice as high as the maximum frequency in the signal to avoid aliasing
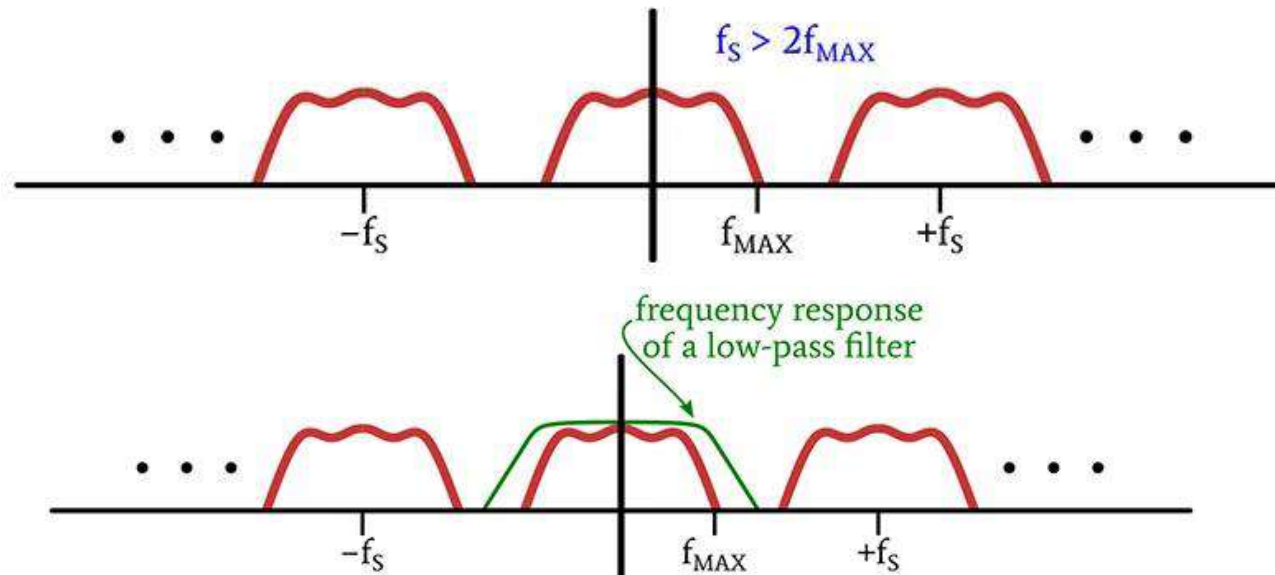
$$F_{\text{sample}} > (2 * F_{\text{signal}})$$




Nyquist rule:

❑ Aliasing $F_{sample} < (2 * F_{signal})$


Sampling and Aliasing

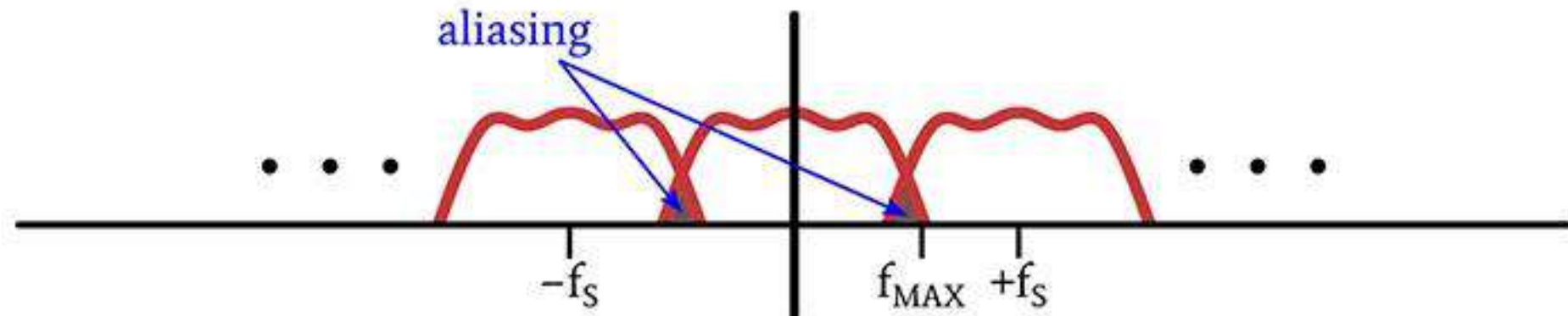- ❑ we see that aliasing happens when the sampling frequency (f_s) is less than twice the maximum signal frequency (f_{max}), we will have overlap in signal.



<https://www.allaboutcircuits.com/technical-articles/the-nyquistshannon-sampling-theorem-exceeding-the-nyquist-rate/>

Example

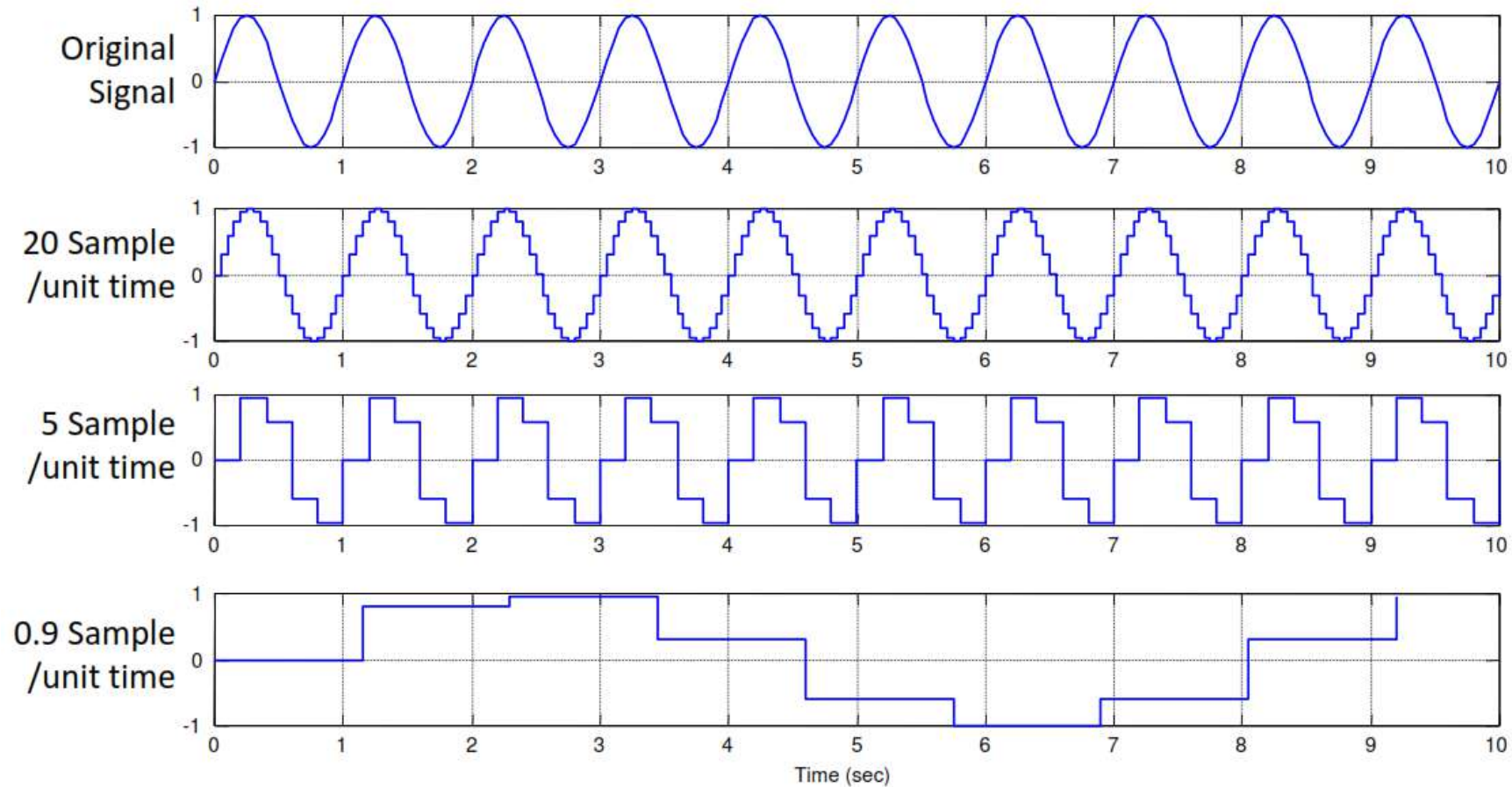

<https://engineering.purdue.edu/ME588/LectureNotes/Unit5b--DAConversion.pdf>

❑ Rule of Thumb

- ❑ For control, sample (20x) faster than signal.
- ❑ For data analysis, sample at least (2x) faster than signal.

Successive Approximation ADC


Conversion Time

- ❑ Maximum $n+1$ clock for an n -bit ADC
- ❑ Fixed conversion time

Serial Output is easily generated

- ❑ Bit decision are made in serial order

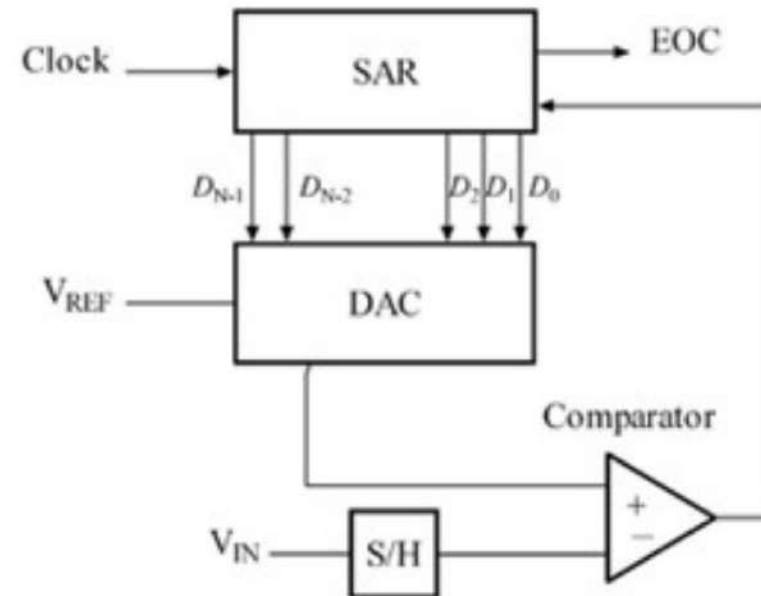- ❑ EOC: End of conversion
- ❑ SAR: Successive Approximation Register
- ❑ V_{REF} : Reference voltage
- ❑ V_{IN} : Input voltage
- ❑ S/H: Sample and hold circuit




Successive Approximation ADC

- Usually used with a Multiplexer– many channel feed to a single converter
- Effective conversion speed for multiplexed ADC depends on number of channels used.

Arduino ADC


6-channel 10-bit ADC

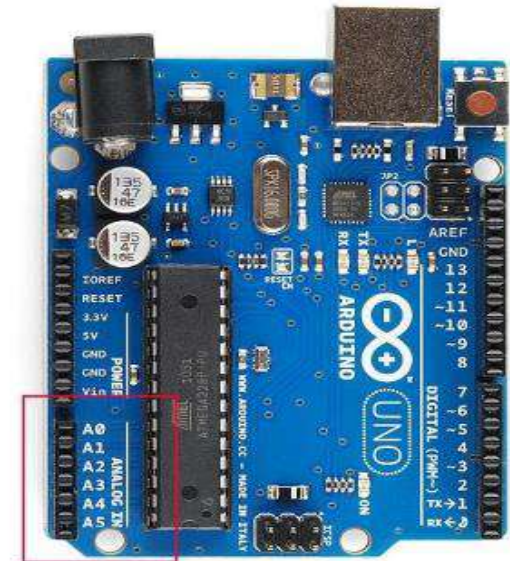


Analog to Digital Converter Flash

1. Uses comparators to determine input voltage range.
2. First type of ADC we can see how a comparator is responsible for each step change.
3. A comparator has two inputs if the positive input is greater the output is a high (1).
4. if the negative input is greater the output is a low (0).

$$V_1 > V_2$$

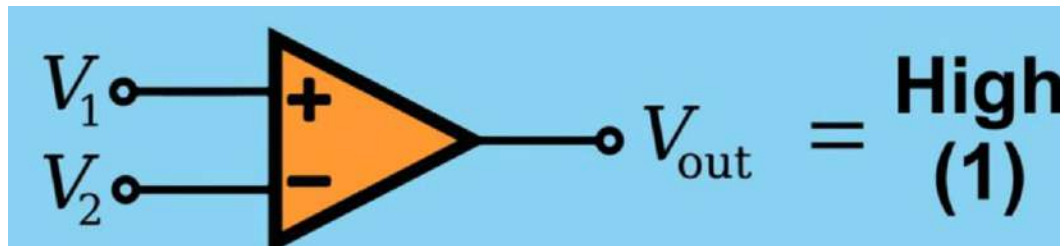


$$V_1 < V_2$$

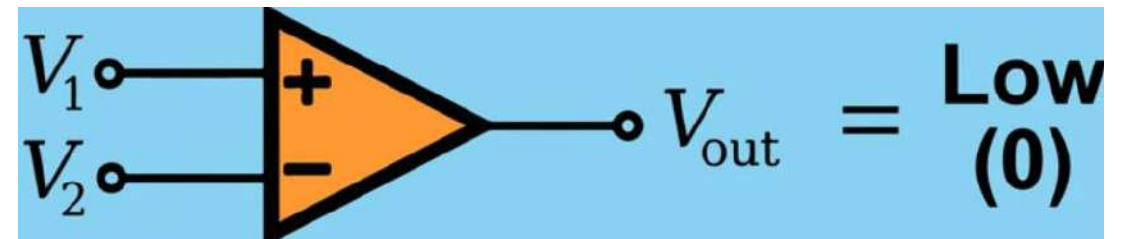


<https://www.youtube.com/watch?v=g4BvbAKNQ90>

3 Bit Flash ADC

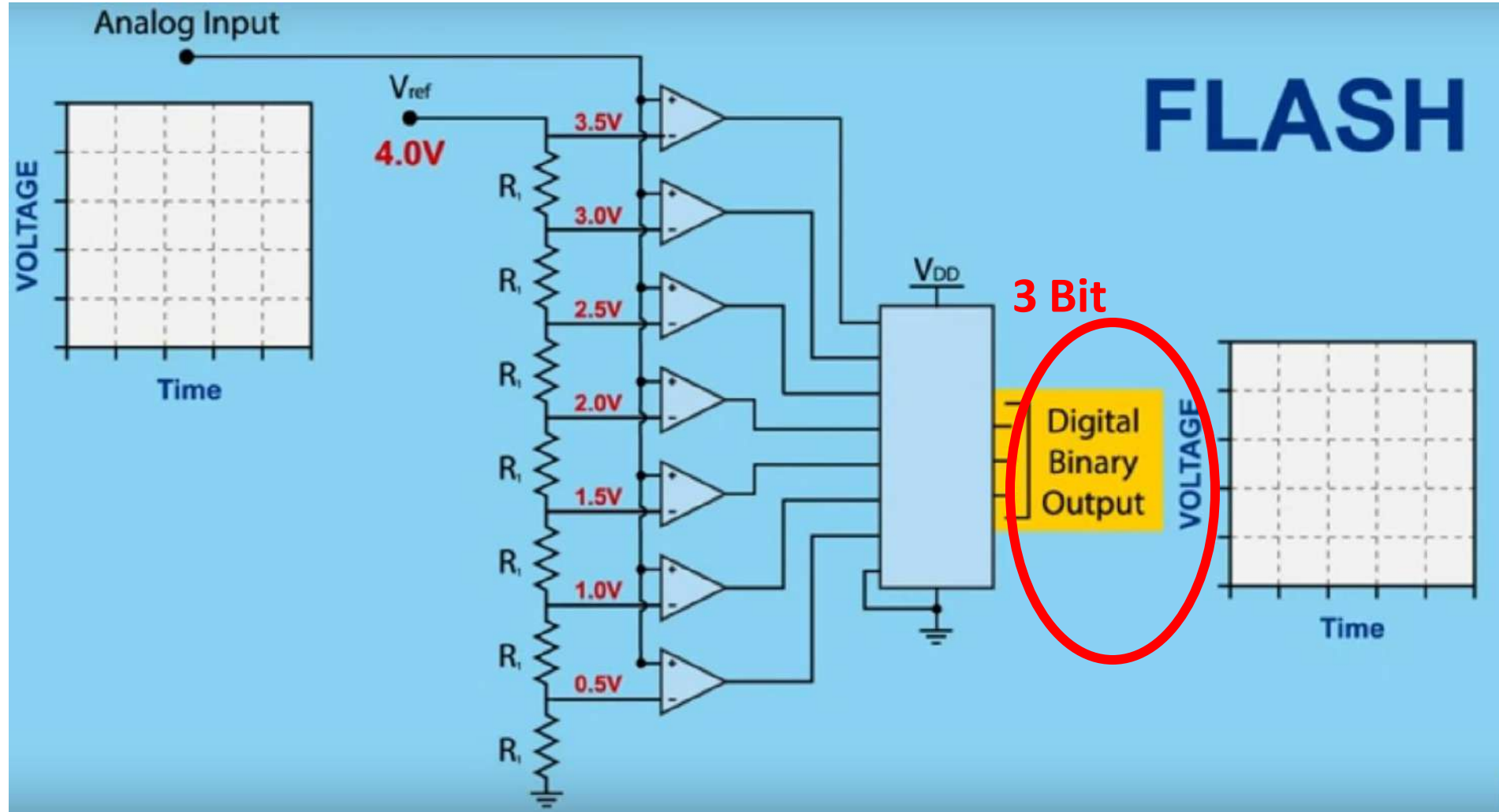

3 Bit Flash ADC

video

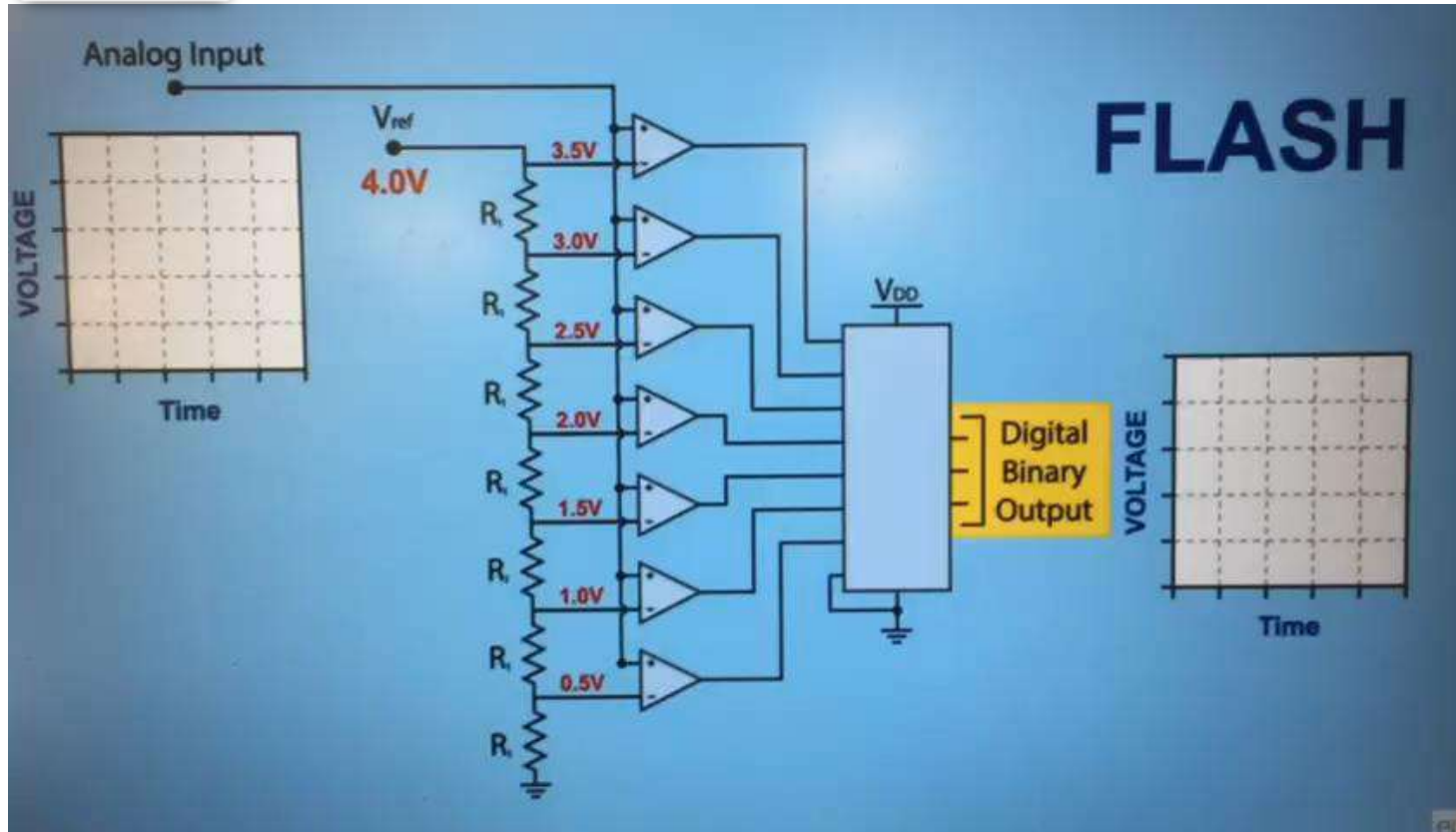


<https://www.youtube.com/watch?v=g4BvbAKNQ90>

Analog to Digital Converter Flash (Direct converter ADC)

□ Also Known as a Parallell ADC

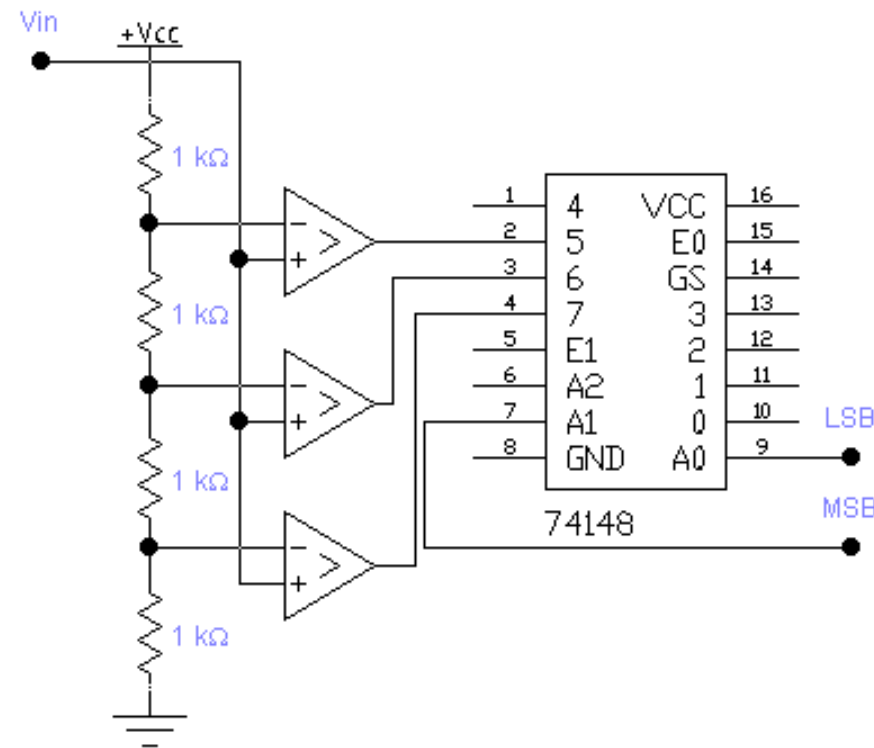1. Uses comparators to determine input voltage range.
2. Gate logic converters comparator output to digital value.
3. Fast; Typical conversion time: 10- 500 nSec





<https://engineering.purdue.edu/ME588/LectureNotes/Unit5b--DAConversion.pdf>

Analog to Digital Converter Flash (Direct converter ADC)

Example: 2 bit Flash ADC

C3	C2	C1	MSB	LSB
0	0	0	0	0
0	0	1	0	1
0	1	0	X	X
0	1	1	1	0
1	0	0	X	X
1	0	1	X	X
1	1	0	X	X
1	1	1	1	1

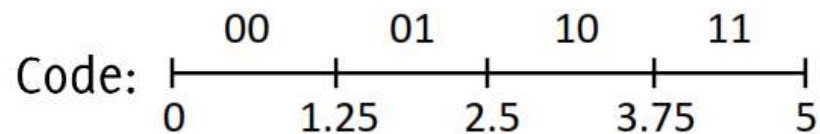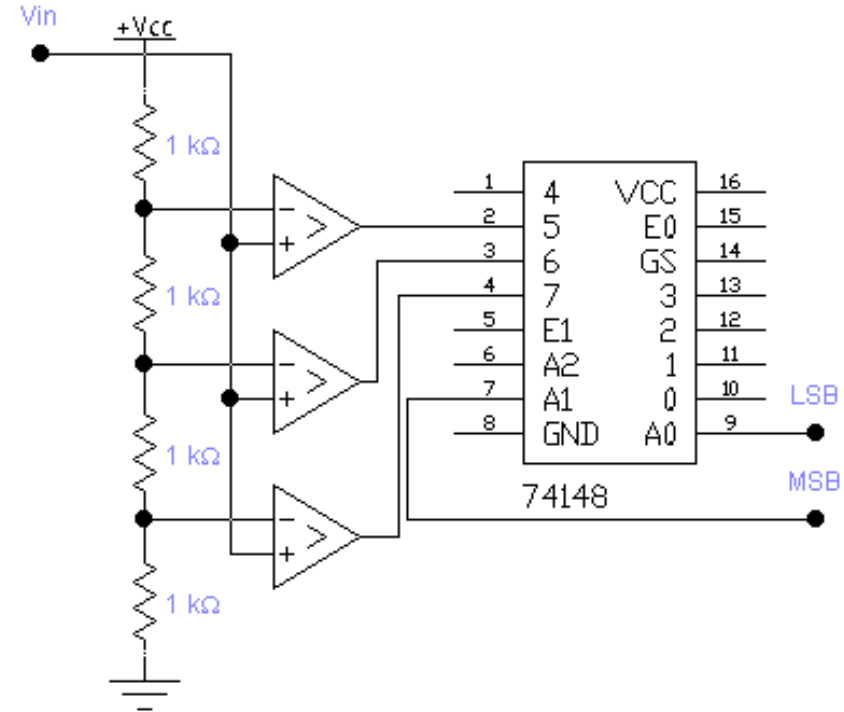

➤ Needs a 3 comparators

C1: $V > 1.25$


C2: $V > 2.5$

C3: $V > 3.75$

ADC is not instantons

Aperture Time

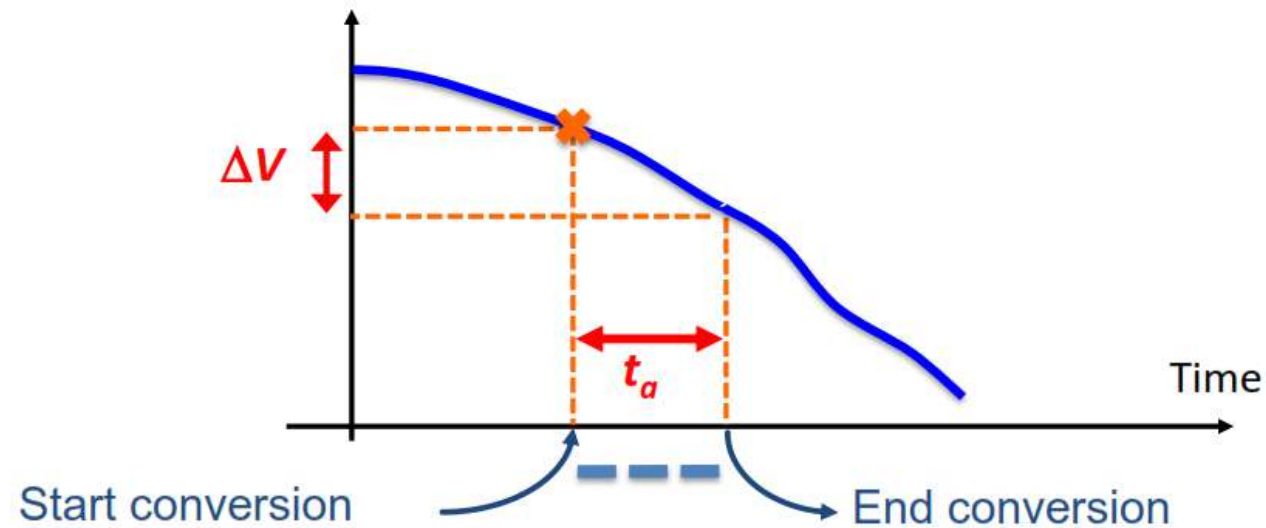- Time needed for an ADC to convert a voltage to a binary code, during which input signal may change.



<https://engineering.purdue.edu/ME588/LectureNotes/Unit5a--ADConversion.pdf>

- Want ΔV to be small.

$$\Delta V < Q$$

Thank You For Your Attention!

Any Question?

