

Digital-to- Analog conversion (DAC)

MEC100x-Lectures 8

Energy, Power and Intelligent Control

School of Electronics, Electrical Engineering and Computer Science

Ashby Building

Queen's University Belfast

Aims


1. Why DAC?
2. DAC Essentials
3. Converter errors
4. R-2R ladder DAC- weighted resistor DAC- Multiplying DAC
5. I/O typical DAC (DAC0808- DAC0807)

ADC and DAC

Digital-to-Analog Conversion (DAC)

- Converts a Digital values to analog outputs of either Voltage or current
- Current DACs require external OP-AMP to convert back to voltage.

0001
0010
0011
0101
....

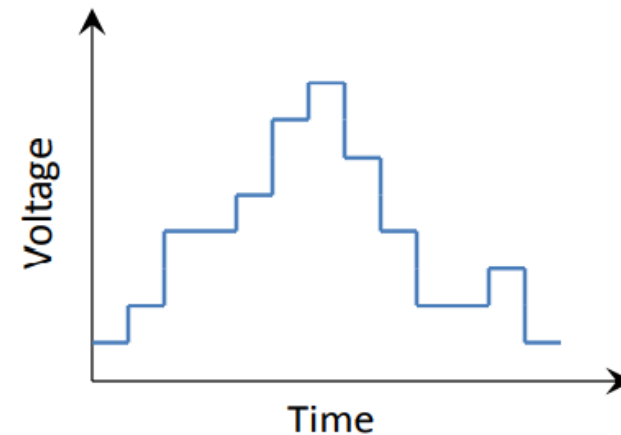

DAC: Digital to Analog Conversion

Analog signals

- ❑ Digital value is stored in a register (latch), then converted.
- ❑ Duration of conversion is called **settling time**.
- ❑ Output of the DAC remains the same until the next value is sent to the register- **a zero-order hold**.

$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot Q$$

Integer equivalent of Binary code

DAC: Digital to Analog Conversion

Mouser.com website...

Digital to analog converter Digital to Analog Converters - DAC

Products (7.153) Datasheets Images Newest Products

Results: 7.153 Smart Filtering










Applied Filters: Semiconductors Data Converter ICs Digital to Analog Converters - DAC

Manufacturer	Series	Resolution	Sampling Rate	Number of Channels	Settling Time	Output Type	Interface Type
---- Most Popular ----	5962	5 bit	500 S/s	1 Channel	1 ns	Buffered Voltage	1-Wire
Analog Devices Inc.	AD1139	6 bit	8 kS/s	1 Channel, 2 Channel	2.2 ns	Current	1-Wire, 2-Wire, 3-W
Texas Instruments	AD3541R	7 bit	12.5 kS/s	2 Channel	4 ns	Current Buffered	2-Wire
Maxim Integrated	AD3542R	8 bit	14.8 kS/s	3 Channel	4.5 ns	Current Buffered, Voltage Buffered	2-Wire, 3-Wire
---- A to Z ----	AD3551R	10 bit	17 kS/s	4 Channel	10 ns	Current Unbuffered	2-Wire, 3-Wire, I2C
Analog Devices Inc.	AD3552R	11 bit	22 kS/s	5 Channel	10.4 ns	Current, Voltage	2-Wire, I2C
Cirrus Logic	AD390	12 bit	33 kS/s	6 Channel	10.5 ns	Voltage	2-Wire, I2C, SMBus
Maxim Integrated	AD4130-8	12 bit, 16 bit	40 kS/s	8 Channel	11 ns	Voltage Buffered	2-Wire, SMBus
Microchip	AD420	13 bit	43 kS/s	9 Channel	11.5 ns	Voltage Unbuffered	3-Wire
Nisshinbo Micro Devices	AD421	14 bit	45 kS/s	10 Channel	12 ns		3-Wire, 4-Wire, DSF
Phoenix Contact	AD5024	16 bit	48 kS/s	12 Channel	13 ns		3-Wire, 4-Wire, I2C
ROHM Semiconductor	AD5025	18 bit	50 kS/s	16 Channel	14 ns		3-Wire, 4-Wire, JES
Renesas Electronics	AD5044	20 bit	55.55 kS/s	32 Channel	15 ns		3-Wire, 4-Wire, Mic
Texas Instruments	AD5045	24 bit	60 kS/s	40 Channel	20 ns		3-Wire, 4-Wire, SPI
	AD5060						3-Wire, DSP, Micro
	AD5061						3-Wire, DSP, Micro


<https://eu.mouser.com/c/semiconductors/data-converter-ics/digital-to-analog-convertersdac/?q=Digital%20to%20analog%20converter>

DAC: Digital to Analog Conversion

Mouser.com website...

<input type="checkbox"/>		<p>Mfr. Part No. MAX538BCSA+</p> <p>Mouser Part No 700-MAX538BCSA</p>	Maxim Integrated	Digital to Analog Converters - DAC +5V, Low-Power, Voltage-Output, Serial 12-Bit DACs	Datasheet	3.226 In Stock	<p>1: 10,85 €</p> <p>10: 9,98 €</p> <p>20: 9,56 €</p> <p>100: 8,42 €</p> <p>200: View</p>	<input type="text"/> <input type="button" value="Buy"/> Min.: 1 Mult.: 1	 Details	
<input type="checkbox"/>		<p>Mfr. Part No. MAX5223EKA+T</p> <p>Mouser Part No 700-MAX5223EKA+T</p>	Maxim Integrated	Digital to Analog Converters - DAC Low-Power, Dual, 8-Bit, Voltage-Output Serial DAC in 8-Pin SOT23	Datasheet	1.402 In Stock	<p>Cut Tape</p> <p>1: 4,54 €</p> <p>10: 4,08 €</p> <p>25: 3,86 €</p> <p>100: 3,34 €</p> <p>250: View</p> <p>Reel</p> <p>2.500: 2,48 €</p> <p>MouseReel Available</p>	<input type="text"/> <input type="button" value="Buy"/> Min.: 1 Mult.: 1 Reel: 2.500	 Details	
<input type="checkbox"/>		<p>Mfr. Part No. DAC43401DSGRQ1</p> <p>Mouser Part No</p>	Texas Instruments	Digital to Analog Converters - DAC Automotive, 8-bit, 1-channel, smart DAC with NVM, buffered voltage output and I2C	Datasheet	3.692 In Stock	<p>Cut Tape</p> <p>1: 1,92 €</p> <p>10: 1,73 €</p>	<input type="text"/> <input type="button" value="Buy"/> Min.: 1	 Details	
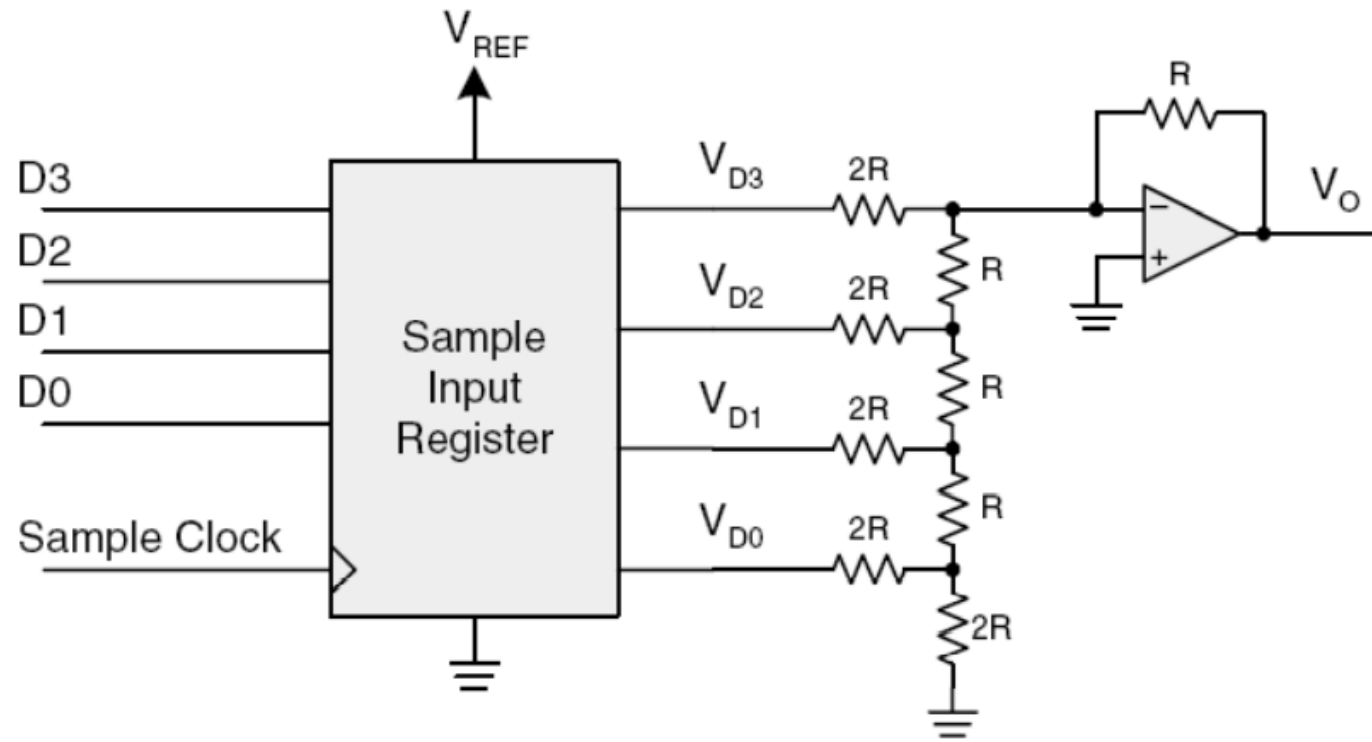
<https://eu.mouser.com/c/semiconductors/data-converter-ics/digital-to-analog-converters-dac/?q=Digital%20to%20analog%20converter>




$$V_O = -V_{REF} \left[\frac{D3}{2} + \frac{D2}{4} + \frac{D1}{8} + \frac{D0}{16} \right]$$

DAC: Digital to Analog Conversion


String DAC

Fast, but needs large number of Resistors

Only one switch closed at a time.

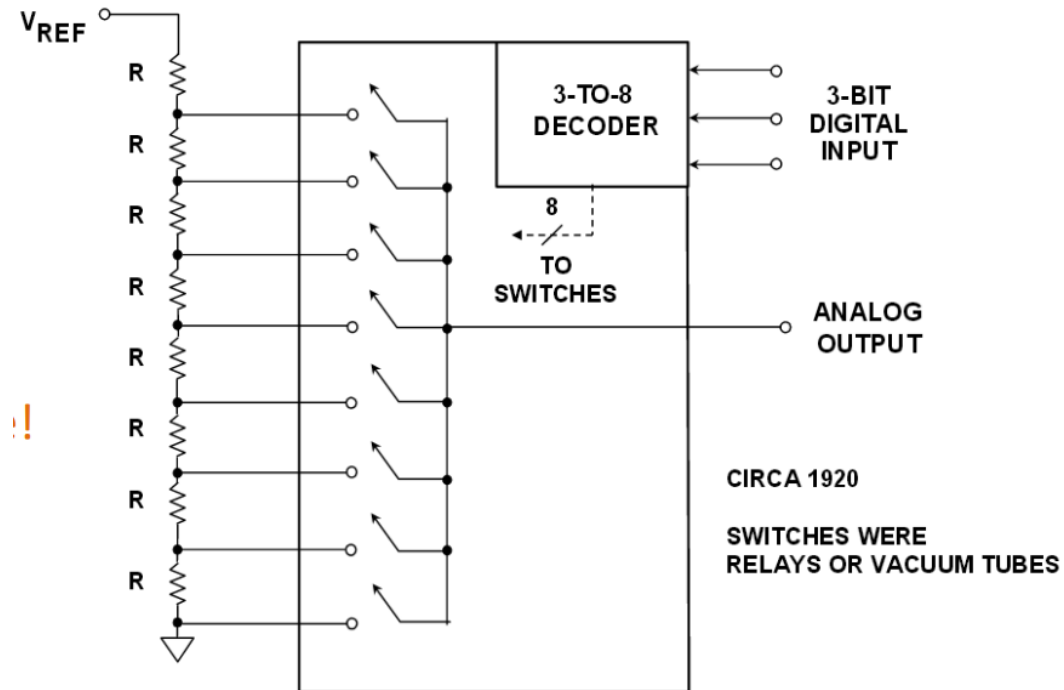

R-2R Ladder DAC (4-bit)

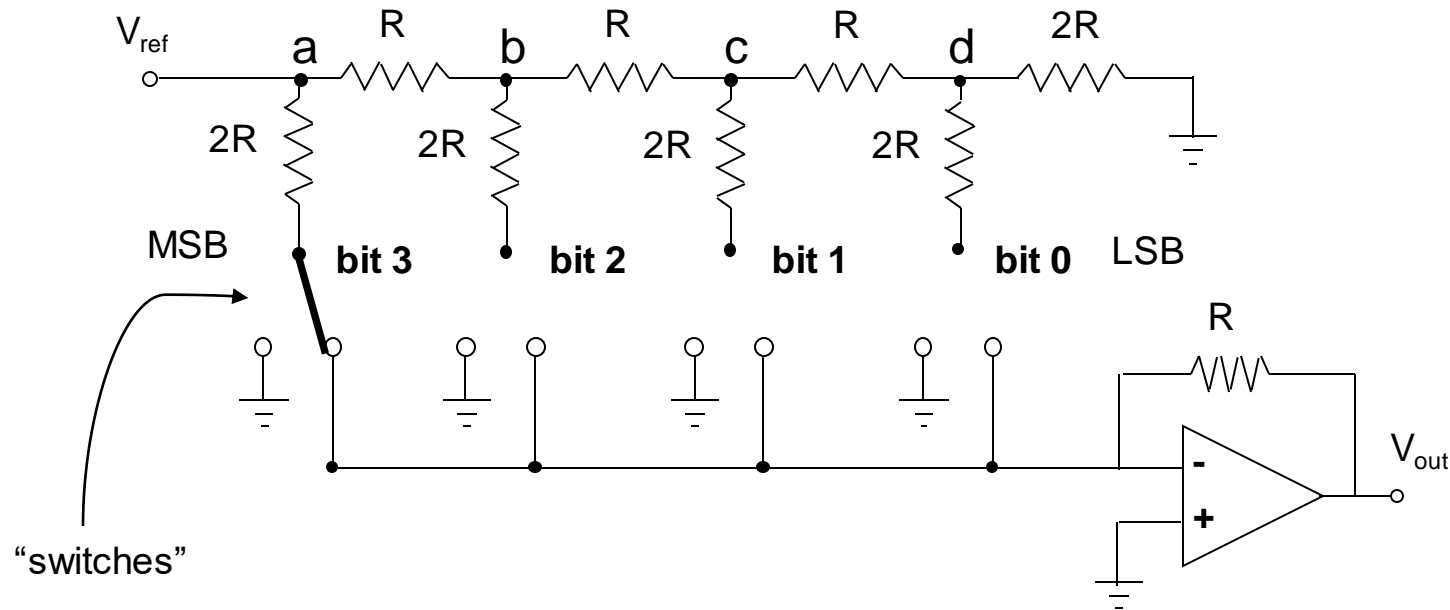

What are the voltages at nodes a - d?


Develop a general expression for V_{out}

$$V_{OUT} = (b_{N-1} \cdot 2^{N-1} + b_{N-2} \cdot 2^{N-2} + \dots + b_1 \cdot 2^1 + b_0 \cdot 2^0) \cdot \frac{V_{REF}}{2^N}$$

Digital to Analog Converter (DAC)

- R-2R Ladder DAC is widely used
 - It's a programmable summing amplifier
 - The smallest change in voltage (the 'resolution') that can be output by the DAC is determined by the number of bits:
 - Resolution = $V_{\text{ref}} / 2^N$, where N is the number of bits
 - Given $V_{\text{ref}} = 5 \text{ V}$, and a 10-bit DAC, what is the smallest change in voltage that the DAC can output?

Problem 1 - Digital-to-Analog Converter

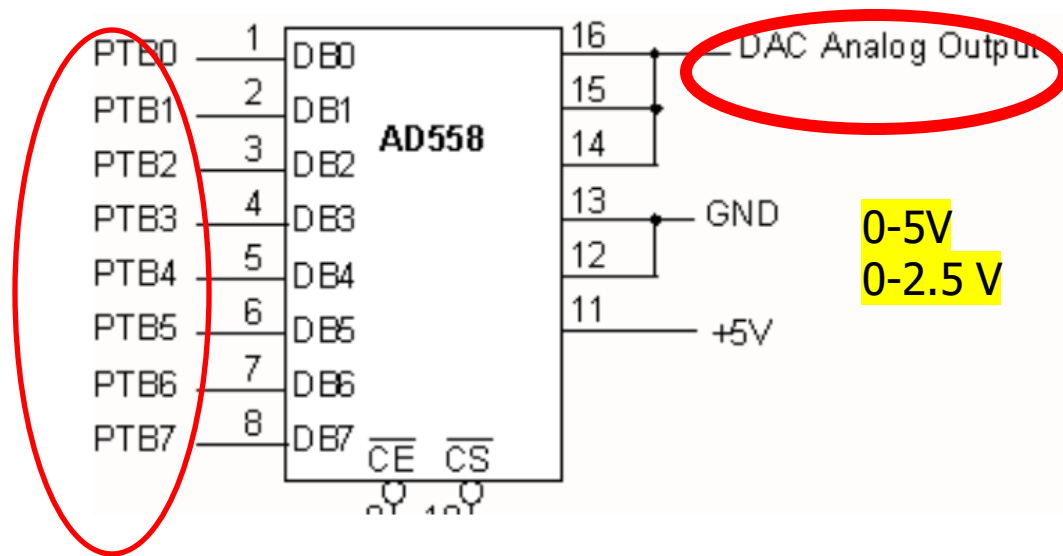


(a) Interface the AD558 8-bit DAC to a parallel port as shown. Write a simple program to exercise the DAC as follows. Generate a saw-tooth ramp by outputting the values from 0 to 255 in a continuous loop. Determine the period and frequency of the output waveform. What information does this reveal about the execution time of your program?


One Channel 0-10V DAC I2C Digital To Analog Converter

**CPU---Micro ===== Analog ===== command Analog actuator---
motor driver/ servo motor driver-- proportional valve
--- induction motor diver ,....**

Dual-In-Line Package

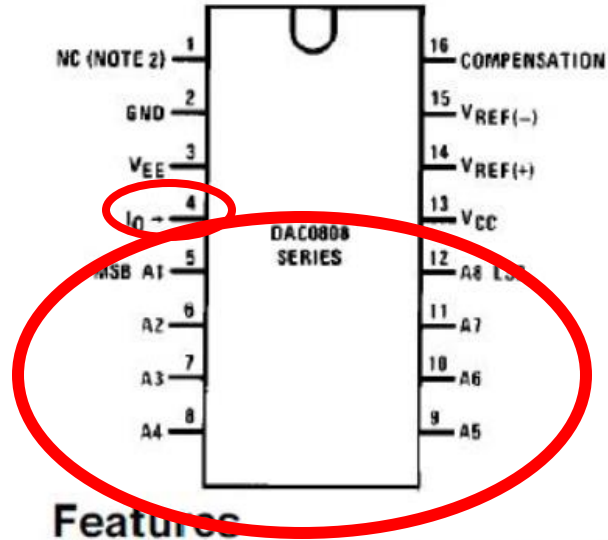


Test Circuits (Continued)

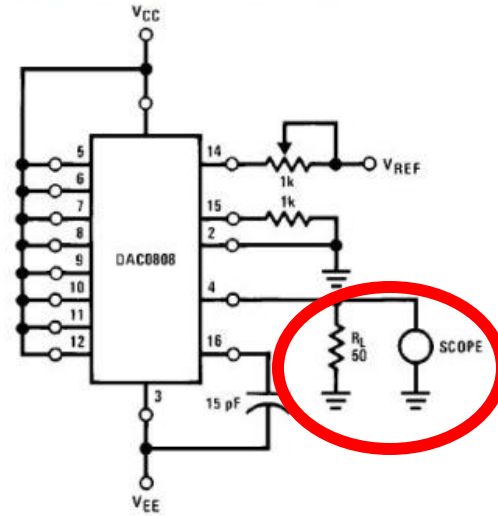

Features

- Relative accuracy: $\pm 0.19\%$ error maximum (DAC0808)
- Full scale current match: ± 1 LSB typ
- 7 and 6-bit accuracy available (DAC0807, DAC0806)
- Fast settling time: 150 ns typ
- Noninverting digital inputs are TTL and CMOS compatible
- High speed multiplying input slew rate: $8 \text{ mA}/\mu\text{s}$
- Power supply voltage range: $\pm 4.5\text{V}$ to $\pm 18\text{V}$
- Low power consumption: 33 mW @ $\pm 5\text{V}$


Differential Amplifier

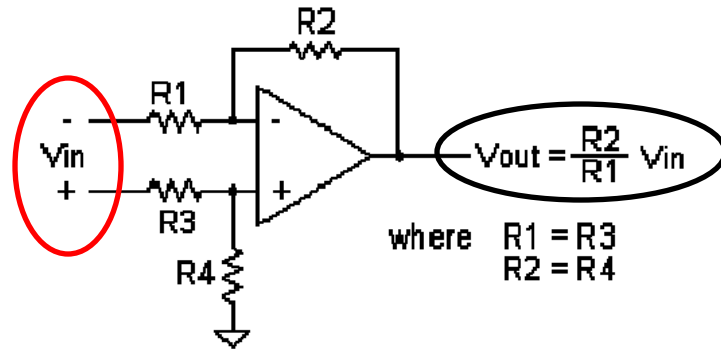

This is the basic circuit from which all others can be derived. All op-amps are designed to amplify the voltage difference between the **non-inverting (+)** and **inverting (-) inputs** while ignoring any **common-mode** signal that may be common to both. The ability to reject the common signal while amplifying the differential input is called the **common-mode rejection ratio (CMRR)**.


Lots of negative feed-back is used to control the voltage gain of the amplifier.

Summing Amplifier

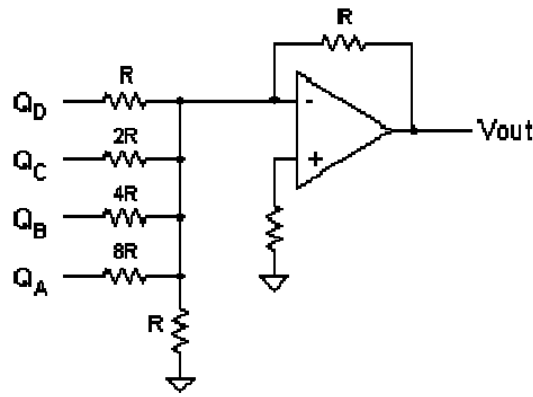

Recall the simple DAC circuit in [Chapter 7, Problem 8](#). By adding an op-amp to the circuit any loading effect on the resistor network is virtually eliminated.

Voltage Comparator

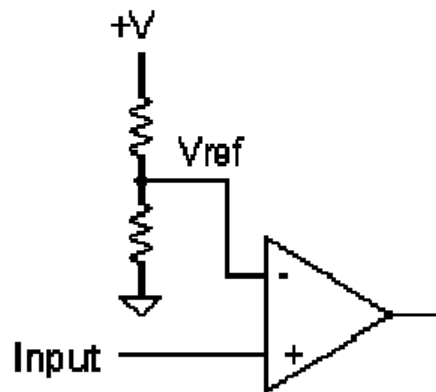

An analog or voltage comparator compares two input voltages and determines which is higher or lower. Since the voltage gain is infinite the output voltage could have only one of two values, equal to the negative or positive supply rail. Thus an input signal with a continuous analog range is converted to a digital signal. This is a 1-bit ADC.

Sampling Theorem


When an analog waveform is sampled, the voltage signal which is continuous in both amplitude and time is digitized. This digitization process results in quantization effects in both domains which lead to important consequences. In the amplitude domain, the resolution is determined by the number of bits of the ADC. Thus an 8-bit ADC can digitize the input signal into 255 voltage steps, equivalent to a precision of 0.4%. The following table shows the effects of various number of ADC bits.

<u>No. of ADC bits</u>	<u>No. of Steps</u>	<u>Precision</u>
8	255	0.4 %
10	1023	0.01 %
12	4095	0.02 %
14	16383	0.006 %
16	65535	0.0015 %

DAC: Digital to Analog Conversion

□ PWM (Pulse Width Modulation)

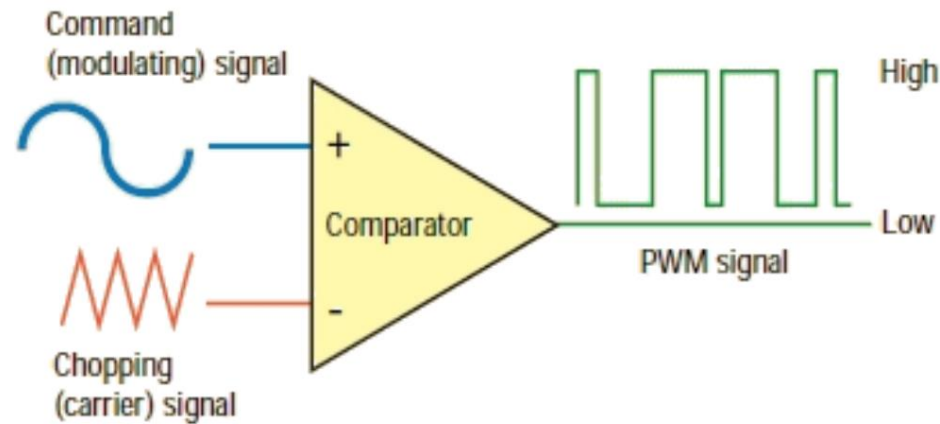
- Rectangular Pulse Wave
- Duty Cycle controls average voltage
- Very high frequency content
- Need a low pass filter to remove the sharp transitions at edges of the pulses
- About 90% efficiency



PWM (Pulse Width Modulation)


$$\text{Duty Cycle} = t_{ON}/T \Rightarrow 0 - 100\%$$

$$\text{Frequency (rad/sec)} = 1/T$$

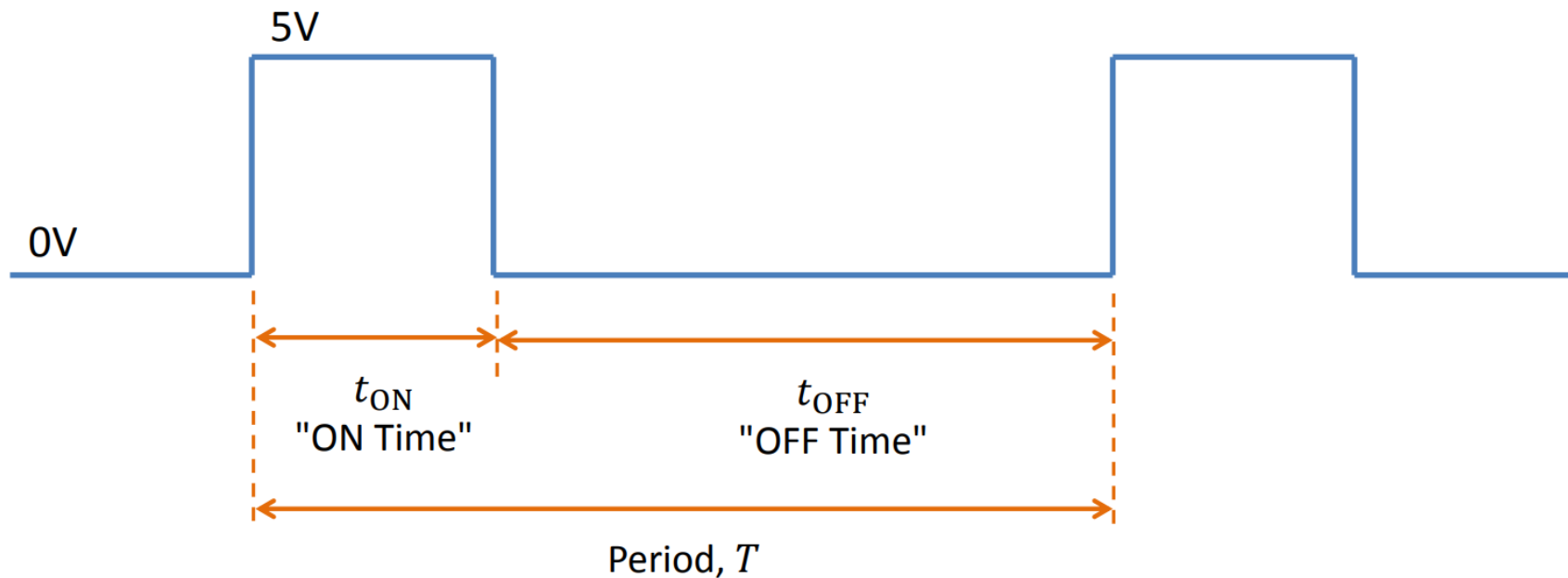

PWM (Pulse Width Modulation)

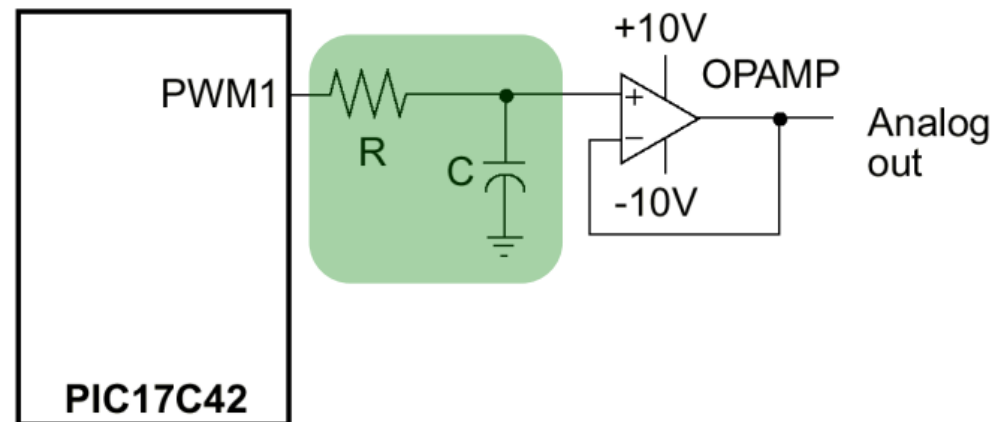- ❑ Low pass filtering the PWM signal can produce an analog signal whose magnitude is proportional to the pulse width of the PWM signal.
- ❑ For Motor/ Motion control, Motor/ Motion system will act as the low pass filter
- ❑ Unipolar output
- ❑ Best suited when an analog output is needed but does not require a high resolution DAC



PWM (Pulse Width Modulation)

8 bit resolution:


100% / 255 \rightarrow 0.39% per step

5V / 255 \rightarrow 19.6 mV per step



Arduino default PWM
frequency:

Pin 5,6 : 976 Hz



Pin 3,9,10,11 : 488 Hz

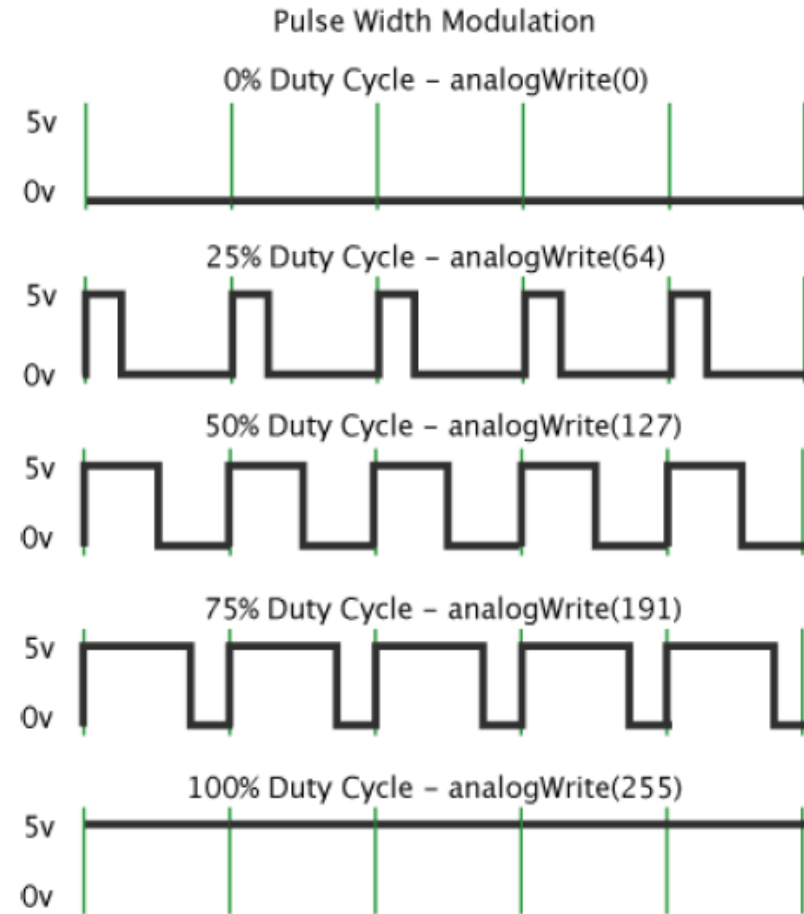


PWM (Pulse Width Modulation)

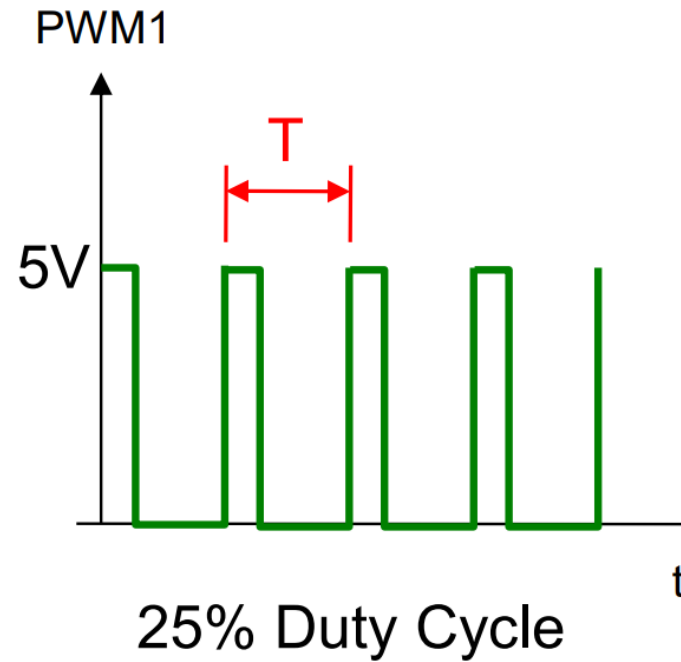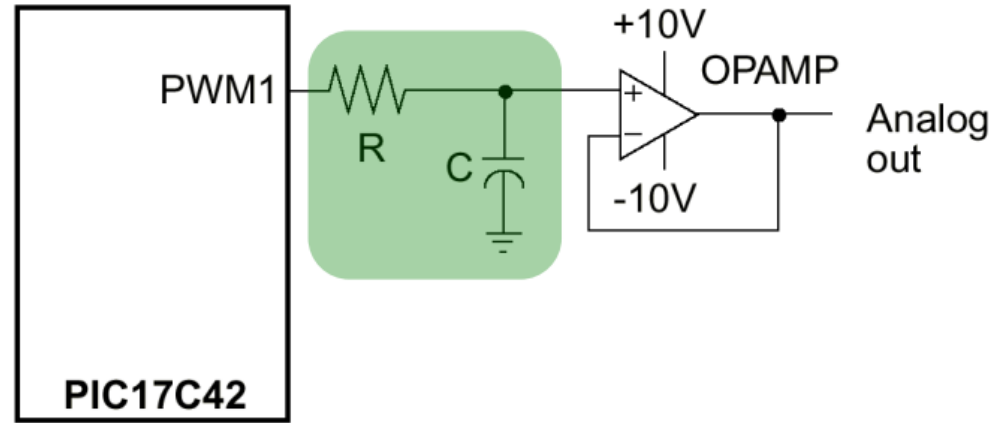


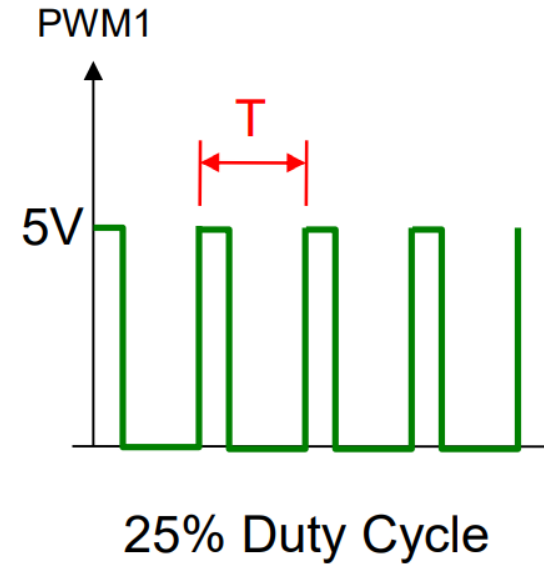
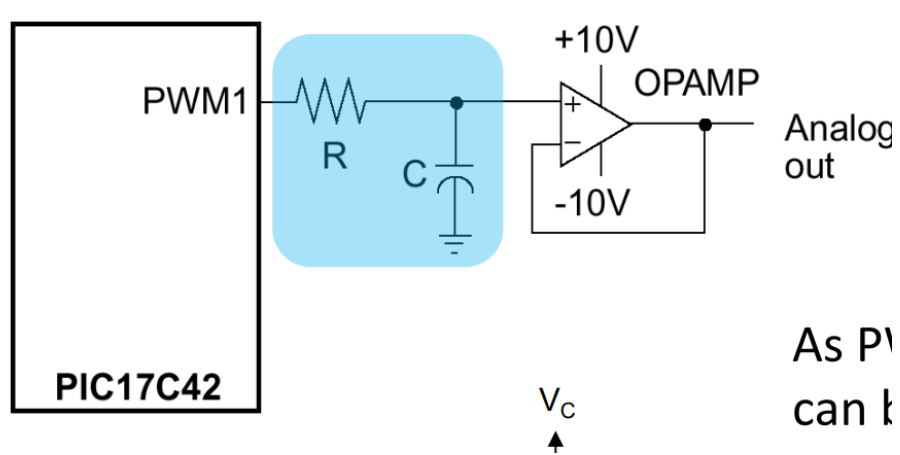
As PWM frequency increases, capacitor can barely charge and discharge fully



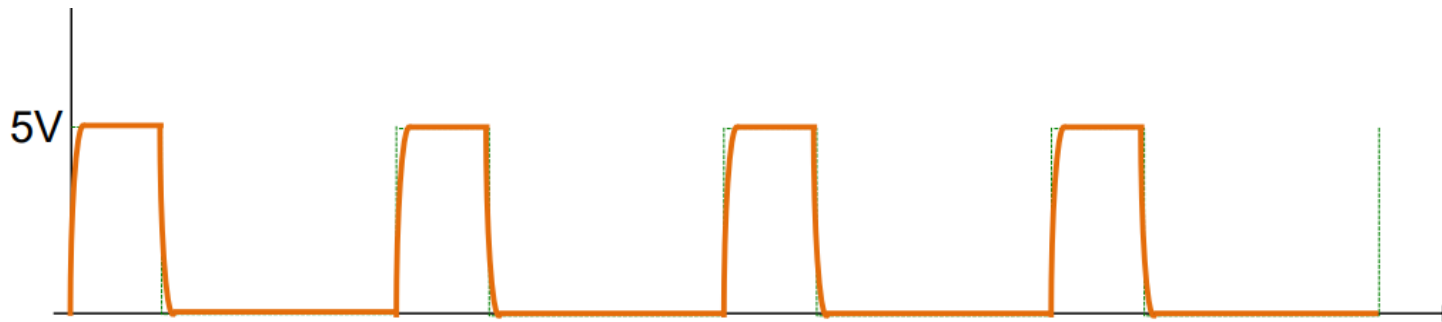
At low PWM frequency, capacitor can fully charge and discharge.



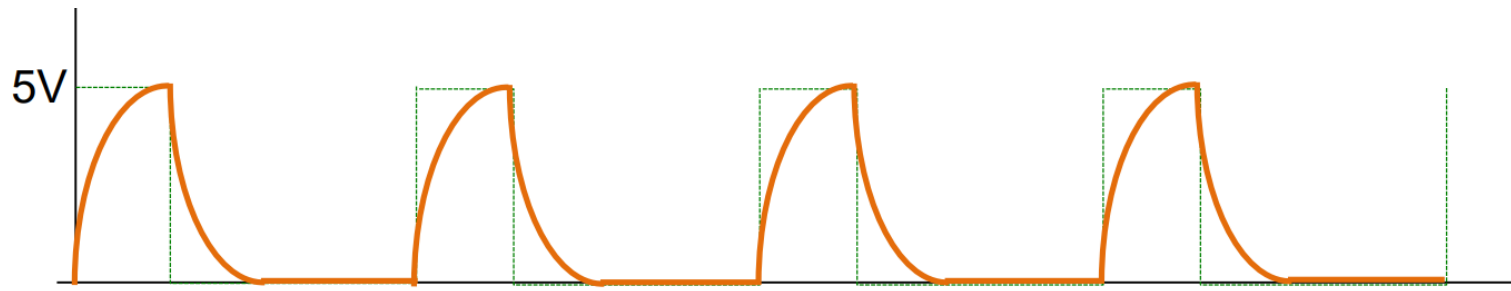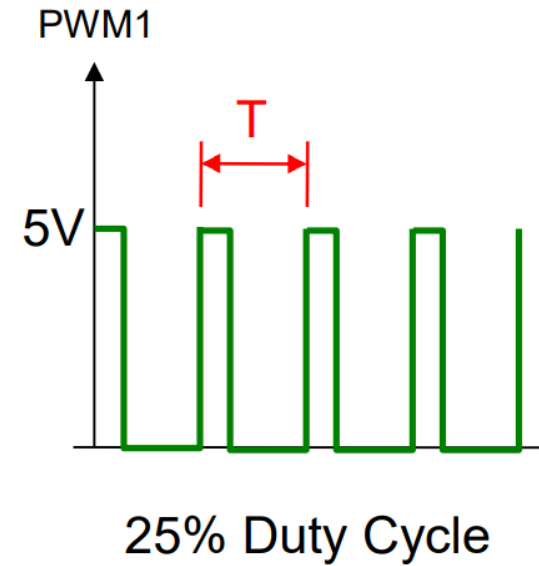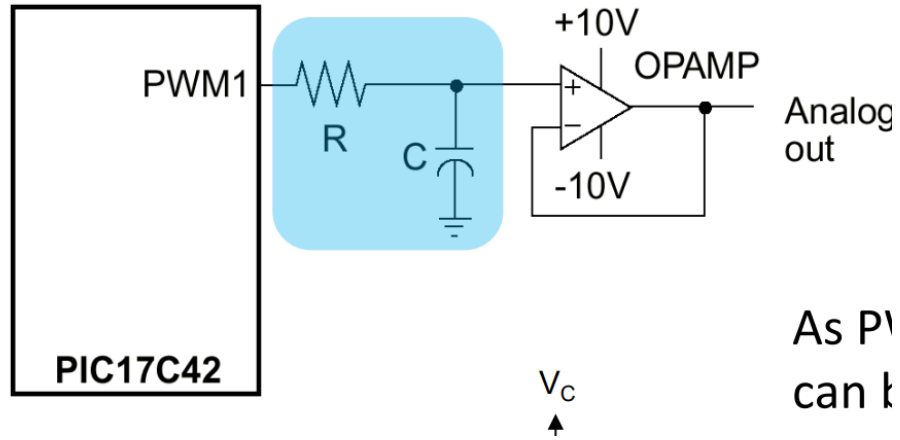As PWM frequency increases, capacitor can barely charge and discharge fully



PWM (Pulse Width Modulation)

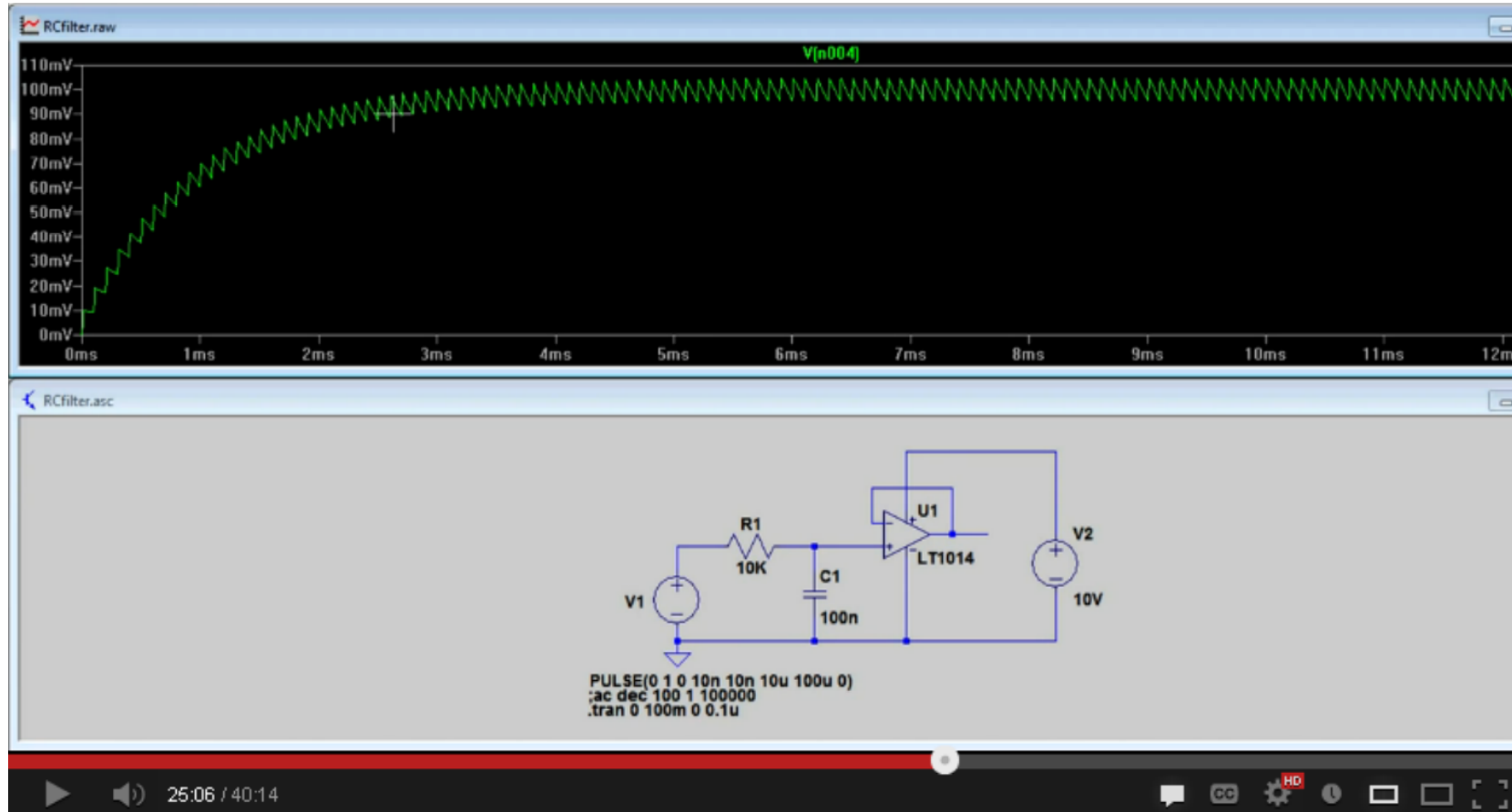

<http://www.youtube.com/watch?v=YaRDbw38x7Q>

Thank You For Your Attention!

Any Question?

